



Technician License Class

1



Technician Class

Chapter 3 Electricity, Components and Circuits

2



Electricity

Current and Voltage.

- Electrons are negatively-charged atomic particles.
- Electric current is the flow of electrons through a material.

3



Electricity

Current and Voltage.

- The magnitude of a current is the number of electrons flowing past a given point in one second.
- Measured in amperes.
 - 1 Ampere = 1 coulomb/second.
 - 1 coulomb \approx 6.24 billion billion (6.24×10^{18}) electrons.
 - Abbreviated to "Amp" or "A".
 - Use symbol "I" in formulas.
- Current is measured using an ammeter.

4



Electricity

Current and Voltage.

- Voltage is the electrical force that causes electrons to flow.
 - a.k.a. – Electromotive force (EMF) or potential.
 - Measured in volts.
 - Abbreviated to “V”
 - Use symbol “E” in formulas
 - Voltage is measured using a voltmeter.

5



Electricity

Current and Voltage.

- Voltage has polarity.
 - Positive voltage attracts electrons.
 - Negative voltage repels electrons.
- Voltage is **always** referenced between 2 points.
 - Surface of the earth is often used as a universal reference point.
 - Called earth ground, ground potential, or ground.

6



Electricity

Current and Voltage.

- Direct and alternating current.
 - If the electrons always flow in the same direction it is called a direct current (DC).
 - If the direction the electrons are flowing reverses it is called an alternating current (AC).
 - A voltage that always has the same polarity is called a direct voltage (V_{DC}).
 - A voltage where the polarity changes is called an alternating voltage (V_{AC}).


7



Electricity

Current and Voltage.

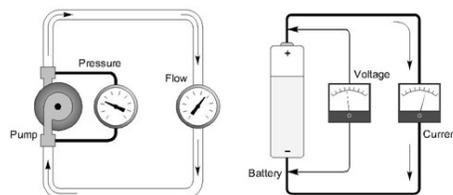- Electrical pressure and flow.
 - The flow of water through a hose or pipe is a good analogy to understand the characteristics of electricity and how they are related.



8

T5A01 -- Electrical current is measured in which of the following units?

- A. Volts
- B. Watts
- C. Ohms
-  D. Amperes

9

T5A03 -- What is the name for the flow of electrons in an electric circuit?

- A. Voltage
- B. Resistance
- C. Capacitance
-  D. Current

10

T5A05 -- What is the electrical term for the force that causes electron flow?

- A. Voltage
- B. Ampere-hours
- C. Capacitance
- D. Inductance

11

T5A09 -- Which of the following describes alternating current?

- A. Current that alternates between a positive direction and zero
- B. Current that alternates between a negative direction and zero
- C. Current that alternates between positive and negative directions
- D. All these answers are correct

12

T7D01 -- Which instrument would you use to measure electric potential?

- A. An ammeter
-  B. A voltmeter
- C. A wavemeter
- D. An ohmmeter

13

T7D04 -- Which instrument is used to measure electric current?

- A. An ohmmeter
- B. A wavemeter
- C. A voltmeter
-  D. An ammeter

14



Electricity

Circuits.

- A circuit is any path where current can flow.
- For current to flow, the circuit must be closed.
 - Current eventually ends up back where it started.
- If only one path, it is a series circuit.
 - Same current flows through all components.
- If multiple paths, it is a parallel circuit.
 - Same voltage is across all components.


15



Electricity

Circuits.

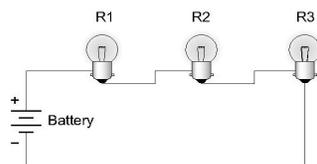- Series circuit.
 - The voltage across each component varies depending on the type and value of each component.
 - The sum of all voltages around the circuit is zero.
 - The same current flows through all components.




16



Electricity

Circuits.

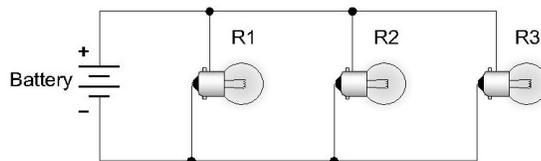- Parallel circuit.
 - The voltage across each component is the same.
 - The sum of all currents in each component equals the total current.
 - The current through each components varies depending on the type and value of the component.




17



Electricity

Circuits.

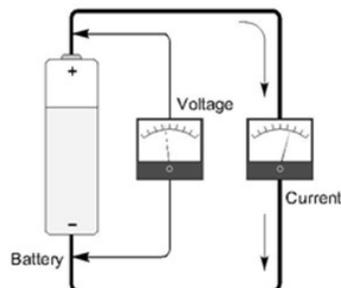- Measuring voltage and current.
 - Voltmeters are always placed in parallel with the circuit.
 - Ammeters are always placed in series with the circuit.



18

T5D13 -- In which type of circuit is current the same through all components?

- A. Series
- B. Parallel
- C. Resonant
- D. Branch

19

T5D14 -- In which type of circuit is voltage the same across all components?

- A. Series
- B. Parallel
- C. Resonant
- D. Branch

20

T7D02 -- How is a voltmeter connected to a component to measure applied voltage?

- A. In series
-  B. In parallel
- C. In quadrature
- D. In phase

21

T7D03 -- When configured to measure current, how is a multimeter connected to a component?

-  A. In series
- B. In parallel
- C. In quadrature
- D. In phase

22



Electricity

Economies of Scale -- The Multimeter

- The most basic piece of test equipment.
 - Everybody should have one.
- Three (or more) instruments in one:
 - Voltmeter
 - Ammeter
 - Ohmmeter
- Measures volts, amperes, and ohms in one package.



23



Electricity

Economies of Scale -- The Multimeter.

- Digital multimeter (DVM)
 - Very inexpensive.
 - Often has extra features in addition to measuring volts, amps, & ohms.



24



Electricity

Economies of Scale -- The Multimeter.

- Meters can only measure current.
 - A voltmeter measures voltage by:
 - Placing a known resistance in parallel with the voltage being measured.
 - Measuring the current through the known resistance.
 - Calculating the voltage using Ohm's law.
 - An ohmmeter measures resistance by:
 - Applying a known voltage to the circuit being measured.
 - Measuring the resulting current.
 - Calculating the resistance using Ohm's law.

25



Electricity

The Multimeter.

- Measuring resistance.
 - **NEVER** attempt to measure resistance with power applied to the circuit.
 - You **WILL** damage your multimeter.
 - **NEVER** attempt to measure voltage with the resistance setting.
 - You **WILL** damage your multimeter.

26



Electricity

The Multimeter.

- When measuring high voltages, make certain that the voltmeter and the test leads are rated for the voltage being measured.
- If a resistance reading is initially low but slowly increases to a higher value, it indicates the presence of a large capacitance in the circuit.

27

T7D06 -- Which of the following can damage a multimeter?

- A. Attempting to measure resistance using the voltage setting
- B. Failing to connect one of the probes to ground
- C. Attempting to measure voltage when using the resistance setting
- D. Not allowing it to warm up properly

28

T7D07 -- Which of the following measurements are made using a multimeter?

- A. Signal strength and noise
- B. Impedance and reactance
-  C. Voltage and resistance
- D. All these choices are correct

29

T7D10 -- What reading indicates that an ohmmeter is connected across a large, discharged capacitor?

-  A. Increasing resistance with time
- B. Decreasing resistance with time
- C. Steady full-scale reading
- D. Alternating between open and short circuit

30

T7D11 -- Which of the following precautions should be taken when measuring circuit resistance with an ohmmeter?

- A. Ensure that the applied voltages are correct
-  B. Ensure that the circuit is not powered
- C. Ensure that the circuit is grounded
- D. Ensure that the circuit is operating at the correct frequency

31

T0A12 -- Which of the following precautions should be taken when measuring high voltages with a voltmeter?

- A. Ensure that the voltmeter has very low impedance
-  B. Ensure that the voltmeter and leads are rated for use at the voltages to be measured
- C. Ensure that the circuit is grounded through the voltmeter
- D. Ensure that the voltmeter is set to the correct frequency

32



Electricity

Resistance and Ohm's Law.

- Resistance
 - The opposition to the flow of electrons.
 - Unit of measurement is the Ohm (Ω).
 - Measured with an ohmmeter.

33



Electricity

Resistance and Ohm's Law.

- Resistance
 - All materials exhibit resistance.
 - Materials with a lot of free electrons (such as metals) have low resistance & are called conductors.
 - Materials with few free electrons (such as glass or rubber) have high resistance & are called insulators.

34

T5A04 -- What are the units of electrical resistance?

- A. Siemens
- B. Mhos
-  C. Ohms
- D. Coulombs

35

T5A07 -- Why are metals generally good conductors of electricity?

- A. They have relatively high density
-  B. They have many free electrons
- C. They have many free protons
- D. All these choices are correct

36

T5A08 -- Which of the following is a good electrical insulator?

- A. Copper
-  B. Glass
- C. Aluminum
- D. Mercury

37

T5A11 -- What type of current flow is opposed by resistance?


- A. Direct current
- B. Alternating current
- C. RF current
-  D. All these choices are correct

38



Electricity

Resistance and Ohm's Law.

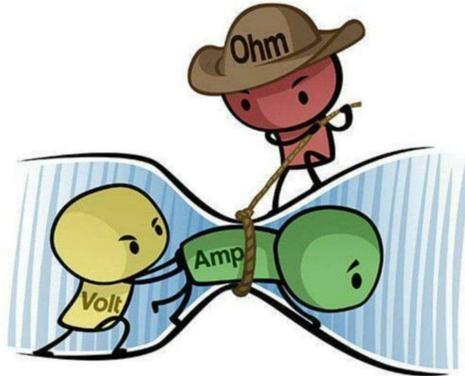

39



Electricity

Resistance and Ohm's Law.

- First published in 1827 by Georg Ohm in his book *“Die galvanische Kette, mathematisch bearbeitet”*
- Mathematically describes the relationship between voltage, current, and resistance.
- Most basic formula in electricity and electronics.


40



Electricity

Resistance and Ohm's Law.

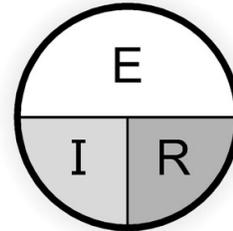- E = Electromotive Force
 - Force causing electrons to flow.
- I = Current Intensity
 - Number of electrons flowing past a point in a given period of time.
- R = Resistance
 - Opposition to flow of electrons.



$$E = I \times R$$

$$I = E/R$$

$$R = E/I$$

41

T5D01 -- What formula is used to calculate current in a circuit?

- A. $I = E \times R$
- B. $I = E / R$
- C. $I = E + R$
- D. $I = E - R$

42

T5D02 -- What formula is used to calculate voltage in a circuit?

- A. $E = I \times R$
- B. $E = I / R$
- C. $E = I + R$
- D. $E = I - R$

43

T5D03 -- What formula is used to calculate resistance in a circuit?

- A. $R = E \times I$
- B. $R = E / I$
- C. $R = E + I$
- D. $R = E - I$

44

T5D04 -- What is the resistance of a circuit in which a current of 3 amperes flows when connected to 90 volts?

- A. 3 ohms
-  B. 30 ohms
- C. 93 ohms
- D. 270 ohms

45

T5D05 -- What is the resistance of a circuit for which the applied voltage is 12 volts and the current flow is 1.5 amperes?

- A. 18 ohms
- B. 0.125 ohms
-  C. 8 ohms
- D. 13.5 ohms

46

T5D06 -- What is the resistance of a circuit that draws 4 amperes from a 12-volt source?

- A. 3 ohms
- B. 16 ohms
- C. 48 ohms
- D. 8 ohms

47

T5D07 -- What is the current in a circuit with an applied voltage of 120 volts and a resistance of 80 ohms?

- A. 9600 amperes
- B. 200 amperes
- C. 0.667 amperes
- D. 1.5 amperes

48

T5D08 -- What is the current through a 100-ohm resistor connected across 200 volts?

- A. 20,000 amperes
- B. 0.5 amperes
-  C. 2 amperes
- D. 100 amperes

49

T5D09 -- What is the current through a 24-ohm resistor connected across 240 volts?

- A. 24,000 amperes
- B. 0.1 amperes
-  C. 10 amperes
- D. 216 amperes

50

T5D10 -- What is the voltage across a 2-ohm resistor if a current of 0.5 amperes flows through it?

- A. 1 volt
- B. 0.25 volts
- C. 2.5 volts
- D. 1.5 volts

51

T5D11 -- What is the voltage across a 10-ohm resistor if a current of 1 ampere flows through it?

- A. 1 volt
- B. 10 volts
- C. 11 volts
- D. 9 volts

52

T5D12 -- What is the voltage across a 10-ohm resistor if a current of 2 amperes flows through it?

- A. 8 volts
- B. 0.2 volts
- C. 12 volts
- D. 20 volts

53



Electricity

Power.


- The rate at which energy is consumed.
 - Any kind of energy – electrical, mechanical, etc.
- Power is measured in watts.
 - Abbreviated "W".
 - Use symbol "P" in formulas.
 - 1 hp \approx 745 watts.
- Power is measured using a wattmeter.

54



Electricity

Power.

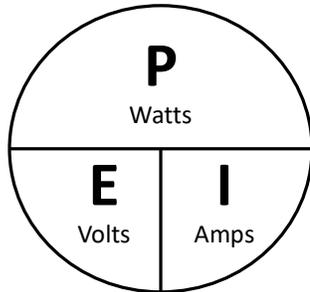

$$P = E \times I$$

$$E = P / I$$

$$I = P / E$$

$$P = E^2 / R$$

$$P = I^2 \times R$$

55

T5A02 -- Electrical power is measured in which of the following units?

- A. Volts
- B. Watts
- C. Watt-hours
- D. Amperes

56

T5A10 -- Which term describes the rate at which electrical energy is used?

- A. Resistance
- B. Current
-  C. Power
- D. Voltage

57

T5C08 -- What is the formula used to calculate electrical power (P) in a DC circuit?

-  A. $P = I \times E$
- B. $P = E / I$
- C. $P = E - I$
- D. $P = I + E$

58

T5C09 -- How much power is delivered by a voltage of 13.8 volts DC and a current of 10 amperes?

- A. 138 watts
- B. 0.7 watts
- C. 23.8 watts
- D. 3.8 watts

59

T5C10 -- How much power is delivered by a voltage of 12 volts DC and a current of 2.5 amperes?

- A. 4.8 watts
- B. 30 watts
- C. 14.5 watts
- D. 0.208 watts

60

T5C11 -- How much current is required to deliver 120 watts at a voltage of 12 volts DC?

- A. 0.1 amperes
- B. 10 amperes
- C. 12 amperes
- D. 132 amperes

61



Components and Units

Basic Components.

- 3 basic types of components:
 - Resistors.
 - Capacitors.
 - Inductors.

62



Components and Units

Basic Components.

- Resistors.
 - A specific amount of a partially conductive material.
 - Oppose flow of electric current.
 - Resistance.
 - Convert electrical energy to heat energy.



63



Components and Units

Basic Components.

- Resistors.
 - Unit of measurement is the ohm (Ω).
 - Values expressed as:
 - Ohms (Ω).
 - Kilohms ($1\text{k}\Omega = 1,000 \Omega$).
 - Megohms ($1\text{M}\Omega = 1,000,000 \Omega$).
 - Values available from $<1 \Omega$ to $>10 \text{M}\Omega$.
 - Maximum power rating in watts (W).
 - $1/8\text{W}$ to several hundred watts.

64



Components and Units

Basic Components.

- Capacitors.
 - Two conductive surfaces separated by an insulator.
 - Temporarily store electrical energy.
 - Stores energy in an electric field.
 - Capacitance.
 - Like a very temporary storage battery.



65



Components and Units

Basic Components.

- Capacitors.
 - Unit of measurement is the farad (F).
 - Values expressed as:
 - Farads (F).
 - Microfarads ($1 \mu\text{F} = 10^{-6} \text{F}$).
 - Picofarads ($1 \text{pF} = 10^{-12} \text{F}$).
 - Values available from 1 pF to >1 F.
 - Maximum voltage rating in volts (V), or kilovolts (kV).
 - Values from a few volts to several kilovolts.


66



Components and Units

Basic Components.

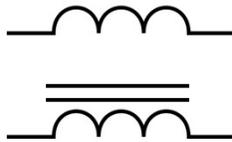- Inductors.
 - A coil of wire, possibly wound on a magnetic core.
 - Temporarily store electrical energy.
 - Stores energy in a magnetic field.
 - Inductance.



67



Components and Units

Basic Components.

- Inductors.
 - Unit of measurement is the henry (H).
 - Values expressed as:
 - Henries (H).
 - Millihenries ($1 \text{ mH} = 10^{-3} \text{ H}$).
 - Microhenries ($1 \mu\text{H} = 10^{-6} \text{ H}$).
 - Values available from $1 \mu\text{H}$ to several Henries.
 - Maximum current rating in milliamps (mA) or amps (A).
 - Values from a few milliamps to several amps.


68



Components and Units

Basic Components.

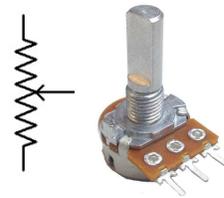- All 3 types of components can be made adjustable.
 - Commonly referred to as “variable”.
- A variable resistor with 3 terminals is often called a “potentiometer”.
 - Commonly shortened to “pot”.
 - Used to adjust voltage or signal level.
 - e.g. – Volume control.



69



Components and Units

Basic Components.

- Transformers.
 - Two or more inductors arranged so that they share their stored magnetic energy.
 - Used to change AC voltage levels.
 - e.g. - Change 120 V_{AC} household voltage to a lower value for use in electronic equipment.




70



Components and Units

Color Code.

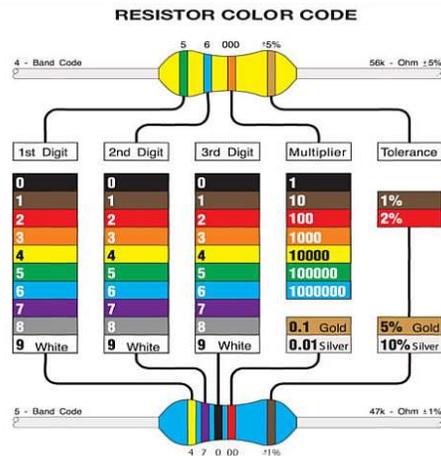

71

T5C01 -- What describes the ability to store energy in an electric field?

- A. Inductance
- B. Resistance
- C. Tolerance
- D. Capacitance

72

T5C02 -- What is the unit of capacitance?

- A. The farad
- B. The ohm
- C. The volt
- D. The henry

73

T5C03 -- What describes the ability to store energy in a magnetic field?

- A. Admittance
- B. Capacitance
- C. Resistance
- D. Inductance

74

T5C04 -- What is the unit of inductance?

- A. The coulomb
- B. The farad
-  C. The henry
- D. The ohm

75

T6A01 -- What electrical component opposes the flow of current in a DC circuit?

- A. Inductor
-  B. Resistor
- C. Voltmeter
- D. Transformer

76

T6A02 -- What type of component is often used as an adjustable volume control?

- A. Fixed resistor
- B. Power resistor
-  C. Potentiometer
- D. Transformer

77

T6A03 -- What electrical parameter is controlled by a potentiometer?

- A. Inductance
-  B. Resistance
- C. Capacitance
- D. Field strength

78

T6A04 -- What electrical component stores energy in an electric field?

- A. Varistor
-  B. Capacitor
- C. Inductor
- D. Diode

79

T6A05 -- What type of electrical component consists of conductive surfaces separated by an insulator?

- A. Resistor
- B. Potentiometer
- C. Oscillator
-  D. Capacitor

80

T6A06 -- What type of electrical component stores energy in a magnetic field?

- A. Varistor
- B. Capacitor
-  C. Inductor
- D. Diode

81

T6A07 -- What electrical component is typically constructed as a coil of wire?

- A. Switch
- B. Capacitor
- C. Diode
-  D. Inductor

82

T6D06 -- What component changes 120 V AC power to a lower AC voltage for other uses?

- A. Variable capacitor
- B. Transformer
- C. Transistor
- D. Diode

83



Components and Units

Reactance and Impedance.

- In circuits containing only resistors, the voltage & current are always “in phase”.
 - Current flow changes at the same time and in the same direction as the voltage change.

84



Components and Units

Reactance and Impedance.

- In circuits containing capacitors or inductors, voltage & current are “out of phase”.
 - Current flow changes before the voltage changes in a capacitor.
 - Current “leads” voltage.
 - Current flow changes after the voltage changes in an inductor.
 - Current “lags” voltage.

85



Components and Units

Reactance and Impedance.



ELI the **ICE** man

86



Components and Units

Reactance and Impedance.

- The opposition to AC current flow in capacitors or inductors is called reactance (X).
 - Reactance (X) is measured in Ohms (Ω).
 - Capacitive reactance (X_C) is measured in Ohms (Ω).
 - Inductive reactance (X_L) is measured in Ohms (Ω).
- The combination of resistance and reactance is called impedance (Z).
 - Impedance (Z) is measured in Ohms (Ω).

87

T5C12 -- What is impedance?

- A. The opposition to AC current flow
- B. The inverse of resistance
- C. The Q or Quality Factor of a component
- D. The power handling capability of a component

88

T5C05 -- What is the unit of impedance?

- A. The volt
- B. The ampere
- C. The coulomb
- D. The ohm

89



Components and Units

Resonance.

- Because current leads voltage in a capacitor & lags voltage in an inductor, a combination of capacitance & inductance exists where the lead time & lag time cancel, resulting in the current & voltage being in phase.
- This condition is called resonance.

90



Components and Units

Resonance.

- Resonant circuit.
 - a.k.a. - Tuned circuit.
 - Acts as filter.
 - Used to adjust frequency of receiver or transmitter.
- The capacitive reactance (X_C) and inductive reactance (X_L) in a resonant circuit are equal.
- Impedance (Z) of a resonant circuit is purely resistive.
 - Reactance = 0Ω .

91

T6D08 -- Which of the following is combined with an inductor to make a resonant circuit?

- A. Resistor
- B. Zener diode
- C. Potentiometer
- D. Capacitor

92

T6D11 -- Which of the following is a resonant or tuned circuit?

- A. An inductor and a capacitor in series or parallel
- B. A linear voltage regulator
- C. A resistor circuit used for reducing standing wave ratio
- D. A circuit designed to provide high-fidelity audio

93



Break



94



Components and Units

Diodes, Transistors, and Integrated Circuits.

- Resistors, capacitors, and inductors are linear devices.
 - Response is **ALWAYS** proportional to the stimulus.

95



Components and Units

Diodes, Transistors, and Integrated Circuits.

- Diodes and transistors are non-linear devices.
 - Response is **NOT** always proportional to the stimulus.

96



Components and Units

Diodes, Transistors, and Integrated Circuits.

- Semi-conductors.
 - Some materials are not good conductors, but are not good insulators either.
 - Silicon, Germanium, etc.

97



Components and Units

Diodes, Transistors, and Integrated Circuits.

- Doping.
 - Adding impurities to certain semi-conductor materials changes their ability to control the flow of current.
 - P-type material.
 - N-type material.

98



Components and Units

Diodes, Transistors, and Integrated Circuits.

- Junctions.
 - When P-type & N-type materials are placed in contact with each other, a “junction” is created.
 - Current will flow easily in one direction through a junction but not in the other direction.

99



Components and Units

Diodes, Transistors, and Integrated Circuits.

- Diodes.
 - The function of the diode is to allow the flow of current in only one direction.
 - Connections named anode & cathode.
 - Cathode is normally identified with a stripe.
 - An analogy is a check valve in a water pipe.


100



Components and Units

Diodes, Transistors, and Integrated Circuits.

- Diodes.

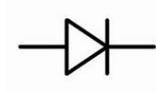

101



Components and Units

Diodes, Transistors, and Integrated Circuits.

- Diodes.
 - High voltage and/or high current diodes designed for use in power supplies are sometimes called “rectifiers”.
 - Convert AC voltage to a varying DC voltage.


102



Components and Units

Diodes, Transistors, and Integrated Circuits.

- Diodes.

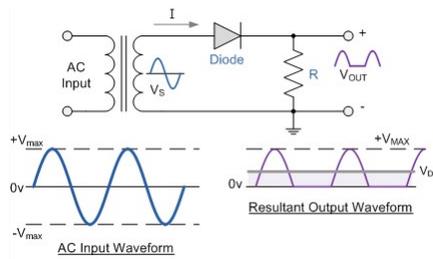


103



Components and Units

Diodes, Transistors, and Integrated Circuits.

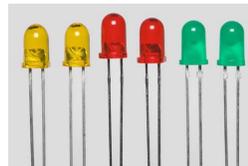- Light-Emitting Diodes (LEDs).
 - Special types of diodes that emit light from the junction when current flows.
 - Color of the light determined by the type of semi-conductor material used.
 - Commonly used as visual indicators.



104



Components and Units

Diodes, Transistors, and Integrated Circuits.

- Forward Voltage Drop.
 - When current is flowing through a junction in the forward direction, there is a voltage drop across the junction.
 - This voltage drop is not affected by the amount of current flowing.

105



Components and Units

Diodes, Transistors, and Integrated Circuits.

- Forward Voltage Drop.
 - The voltage drop is different for different types of materials.
 - Germanium = ~0.3 volts.
 - Silicon = ~0.7 volts.
 - LEDs = ~1.2 to 1.5 volts.

106



Components and Units

Diodes, Transistors, and Integrated Circuits.

- Transistors.
 - Have 3 layers of material & 2 junctions.
 - N-P-N.
 - P-N-P.



107



Components and Units

Diodes, Transistors, and Integrated Circuits.

- Transistors.
 - Bipolar Transistors.
 - Connections named Emitter, Base, & Collector.
 - Small change in base current results in large change in emitter current.
 - Low input impedance.
 - Low output impedance.



108



Components and Units

Diodes, Transistors, and Integrated Circuits.

- Transistors.
 - Bipolar Transistors.

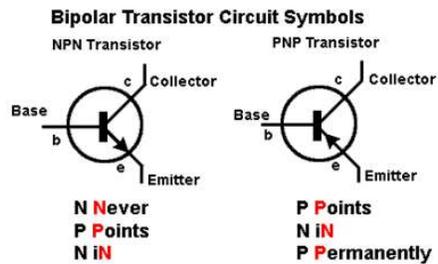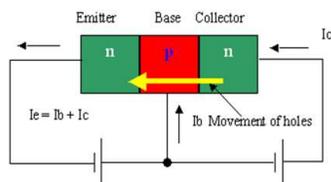

109



Components and Units

Diodes, Transistors, and Integrated Circuits.

- Transistors.
 - Field-Effect Transistors (FETs).
 - Connections named Source, Drain, & Gate.
 - Change in gate voltage results in change in drain current.
 - High input impedance.
 - Low output impedance.



110




Components and Units

Diodes, Transistors, and Integrated Circuits.

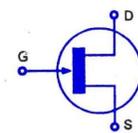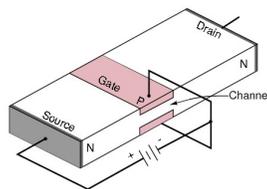- Transistors.
 - Field-Effect Transistors (FETs).



N-Channel JFET

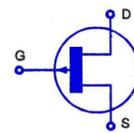

P-Channel JFET

111



Components and Units

Diodes, Transistors, and Integrated Circuits.

- Transistors.
 - Both bipolar transistors and FETs can be used to amplify signals.
 - Gain.
 - Both bipolar transistors and FETs can be used to turn signals on or off.
 - Electronic switch.

112



Components and Units

Diodes, Transistors, and Integrated Circuits.

- Integrated circuits.
 - A collection of components contained in one device that accomplishes a specific task.
 - Acts like a “black-box”.



113

T6B01 Which is true about forward voltage drop in a diode?

- A. It is lower in some diode types than in others
- B. It is proportional to peak inverse voltage
- C. It indicates that the diode is defective
- D. It has no impact on the voltage delivered to the load

114

T6B02 -- What electronic component allows current to flow in only one direction?

- A. Resistor
- B. Fuse
-  C. Diode
- D. Driven element

115

T6B03 -- Which of these components can be used as an electronic switch?

- A. Varistor
- B. Potentiometer
-  C. Transistor
- D. Thermistor

116

T6B04 -- Which of the following components can consist of three regions of semiconductor material?

- A. Alternator
-  B. Transistor
- C. Triode
- D. Pentagrid converter

117

T6B05 -- What type of transistor has a gate, drain, and source?

- A. Varistor
-  B. Field-effect
- C. Tesla-effect
- D. Bipolar junction

118

T6B06 -- How is the cathode lead of a semiconductor diode often marked on the package?

- A. With the word "cathode"
-  B. With a stripe
- C. With the letter C
- D. With the letter K

119

T6B07 -- What causes a light-emitting diode (LED) to emit light?

-  A. Forward current
- B. Reverse current
- C. Capacitively-coupled RF signal
- D. Inductively-coupled RF signal

120

T6B08 -- What does the abbreviation FET stand for?

- A. Frequency Emission Transmitter
- B. Fast Electron Transistor
- C. Free Electron Transmitter
-  D. Field Effect Transistor

121

T6B09 -- What are the names for the electrodes of a diode?

- A. Plus and minus
- B. Source and drain
-  C. Anode and cathode
- D. Gate and base

122

T6B10 -- Which of the following can provide power gain?

- A. Transformer
-  B. Transistor
- C. Reactor
- D. Resistor

123

T6B11 -- What is the term that describes a device's ability to amplify a signal?

-  A. Gain
- B. Forward resistance
- C. Forward voltage drop
- D. On resistance

124

T6B12 -- What are the names of the electrodes of a bipolar junction transistor?

- A. Signal, bias, power
-  B. Emitter, base, collector
- C. Input, output, supply
- D. Pole one, pole two, output

125

T6D01 -- Which of the following devices or circuits changes an alternating current into a varying direct current signal?

- A. Transformer
-  B. Rectifier
- C. Amplifier
- D. Reflector

126

T6D07 -- Which of the following is commonly used as a visual indicator?

- A. LED
- B. FET
- C. Zener diode
- D. Bipolar transistor

127

T6D09 -- What is the name of a device that combines several semiconductors and other components into one package?

- A. Transducer
- B. Multi-pole relay
- C. Integrated circuit
- D. Transformer

128

T6D10 -- What is the function of component 2 in Figure T-1?

- A. Give off light when current flows through it
- B. Supply electrical energy
- C. Control the flow of current**
- D. Convert electrical energy into radio waves

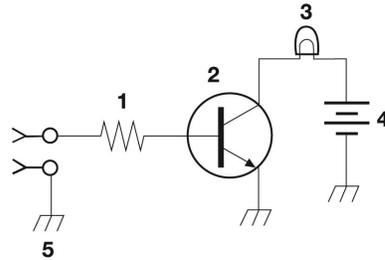


Figure T-1

129



Components and Units

Protective Components.

- Used to prevent or limit damage and safety hazards.
 - Fuse.
 - Circuit breaker.
 - Ground fault circuit interrupter (GFCI).
 - Surge protectors.
 - Lightning arrestors.

130



Components and Units

Protective Components.

- Fuses blow.
 - One-time protection.
 - A piece of metal melts when the maximum current is exceeded.



131



Components and Units

Protective Components.

- Circuit breakers trip.
 - Use a bi-metallic strip or an electromagnet to open circuit when the maximum current is exceeded.
 - Can be reset & reused.




132



Components and Units

Protective Components.

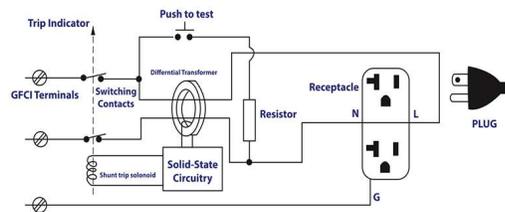- Ground fault circuit interrupter (GFCI).
 - Opens the circuit if the current flowing into a device is not equal to the current flowing out of the device.
 - Can be reset & reused.



133



Components and Units

Protective Components.

- Surge protectors.
 - Limit transient voltage spikes.
 - AC power lines (outlet strips).
 - Telephone wiring.
- Lightning arrestors.
 - Limit transient voltage spikes.
 - Antenna feed lines.

134

T6A09 -- What electrical component is used to protect other circuit components from current overloads?

- A. Fuse
- B. Thyatron
- C. Varactor
- D. All these choices are correct

135

T0A04 -- What is the purpose of a fuse in an electrical circuit?

- A. To prevent power supply ripple from damaging a component
- B. To remove power in case of overload
- C. To limit current to prevent shocks
- D. All these choices are correct

136

T0A05 -- Why should a 5-ampere fuse never be replaced with a 20-ampere fuse?

- A. The larger fuse would be likely to blow because it is rated for higher current
- B. The power supply ripple would greatly increase
- C. Excessive current could cause a fire
- D. All of these choices are correct

137



Components and Units

Circuit gatekeepers.

- Switches and relays are used to control the flow of current through a circuit.
 - Turn current flow off
 - a.k.a. – Opening the circuit.
 - Turn current flow on
 - a.k.a. – Closing the circuit.
 - Make the current take a different path.






138



Components and Units

Circuit gatekeepers.

- Switches.
 - Manually operated.

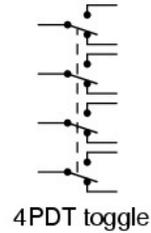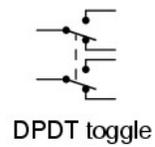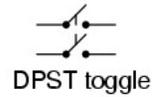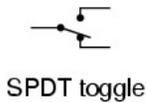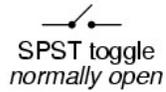



139



Components and Units

Circuit gatekeepers.

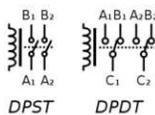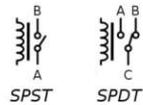- Relays.
 - An electrically-controlled switch.
 - A set of switch contacts connected to an electromagnet.



140

T6A08 -- What is the function of an SPDT switch?

- A. A single circuit is opened or closed
- B. Two circuits are opened or closed
- C. A single circuit is switched between one of two other circuits
- D. Two circuits are each switched between one of two other circuits

141

T6A12 -- What type of switch is represented by component 3 in figure T-2?

- A. Single-pole single-throw
- B. Single-pole double-throw
- C. Double-pole single-throw
- D. Double-pole double-throw

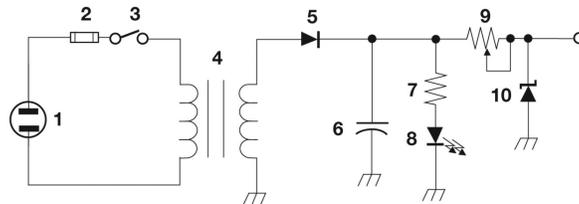


Figure T-2

142

T6D02 -- What is a relay?

- A. An electrically-controlled switch
- B. A current controlled amplifier
- C. An inverting amplifier
- D. A pass transistor

143



Components and Units

Indicators, Meters, and Displays.

- An indicator displays on/off status.
- A meter shows a value on a numeric scale.
- A display consists of several indicators and/or meters.



144

T6D04 -- Which of the following displays an electrical quantity as a numeric value?

- A. Potentiometer
- B. Transistor
- C. Meter
- D. Relay


145



Components and Units

Schematics and Component Symbols.

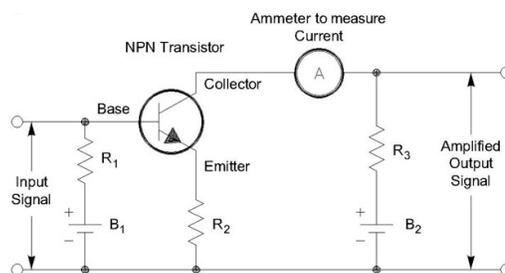- A schematic diagram portrays how components are connected together to form a circuit.



146



Components and Units

Schematics and Component Symbols.

- Schematic diagrams:
 - **DO** use a set of standard symbols for each component in a circuit.
 - **DO** represent the way components are interconnected.
 - **DO NOT** represent the physical layout of the components.
 - **DO NOT** represent the length of the conductors used for the interconnections.


147



Components and Units

Schematics and Component Symbols.

- Component symbols.

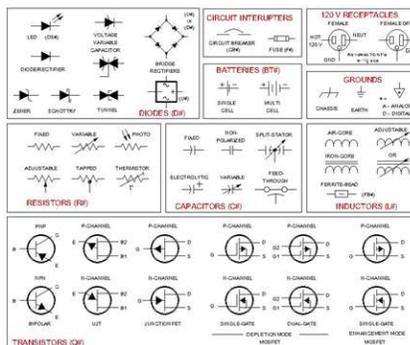

148

T6C01 -- What is the name of an electrical wiring diagram that uses standard component symbols?

- A. Bill of materials
- B. Connector pinout
- C. Schematic
- D. Flow chart

149

T6C02 -- What is component 1 in figure T-1?

- A. Resistor
- B. Transistor
- C. Battery
- D. Connector

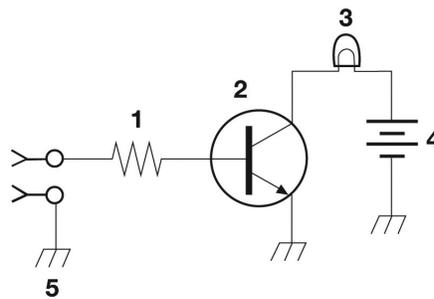


Figure T-1

150

T6C03 -- What is component 2 in figure T-1?

- A. Resistor
- B. Transistor
- C. Indicator lamp
- D. Connector

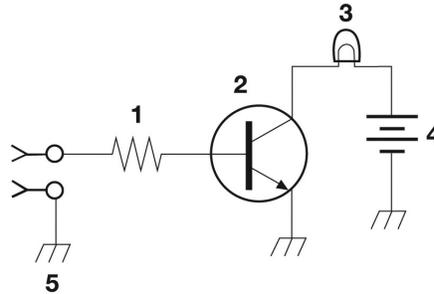


Figure T-1

151

T6C04 -- What is component 3 in figure T-1?

- A. Resistor
- B. Transistor
- C. Lamp
- D. Ground symbol

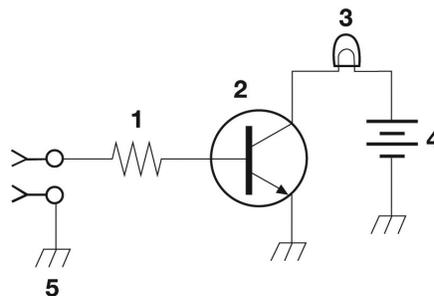


Figure T-1

152

T6C05 -- What is component 4 in figure T-1?

- A. Resistor
- B. Transistor
- C. Ground symbol
- D. Battery

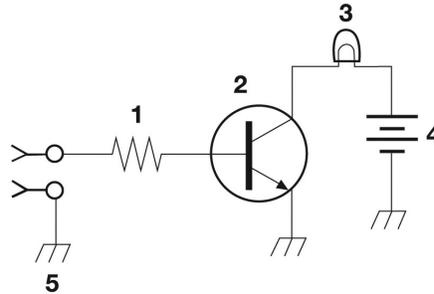


Figure T-1

153

T6C06 -- What is component 6 in figure T-2?

- A. Resistor
- B. Capacitor
- C. Regulator IC
- D. Transistor

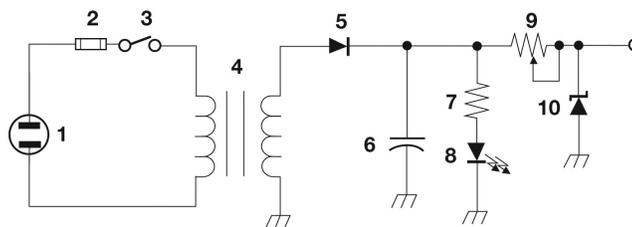


Figure T-2

154

T6C07 -- What is component 8 in figure T-2?

- A. Resistor
- B. Inductor
- C. Regulator IC
- ➔ D. Light emitting diode

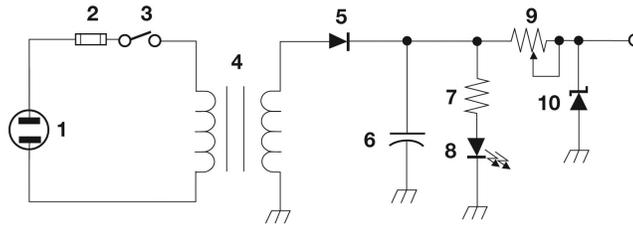


Figure T-2

155

T6C08 -- What is component 9 in figure T2?

- A. Variable capacitor
- B. Variable inductor
- ➔ C. Variable resistor
- D. Variable transformer

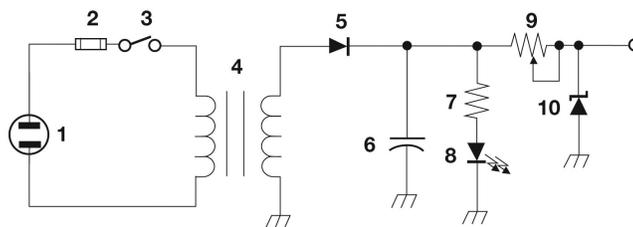


Figure T-2

156

T6C09 -- What is component 4 in figure T2?

- A. Variable inductor
- B. Double-pole switch
- C. Potentiometer

→ D. Transformer

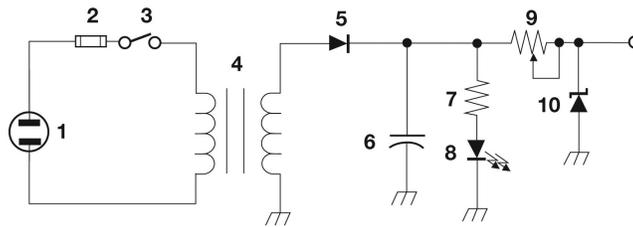


Figure T-2

157

T6C10 -- What is component 3 in figure T-3?

- A. Connector
- B. Meter
- C. Variable capacitor

→ D. Variable inductor

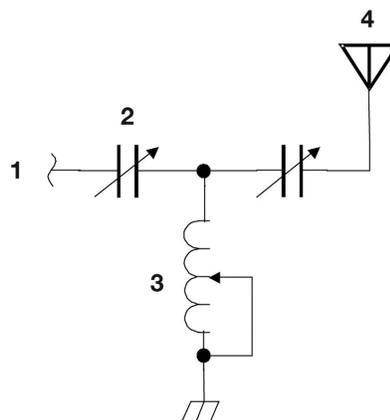


Figure T-3

158

T6C11 -- What is component 4 in figure T-3?

- A. Antenna
- B. Transmitter
- C. Dummy load
- D. Ground

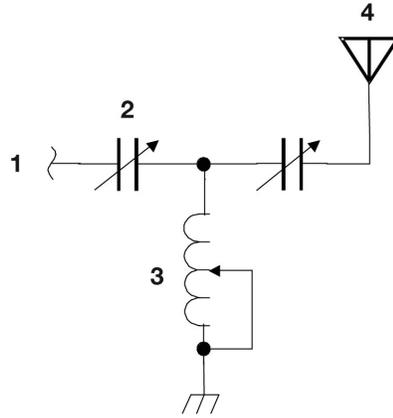


Figure T-3

159

T6C12 -- Which of the following is accurately represented in electrical schematics?

- A. Wire lengths
- B. Physical appearance of components
- C. Component connections
- D. All these choices are correct

160



Radio Circuits

Oscillators and Amplifiers.

- Oscillators produce a low-power signal at a specific frequency.
 - Used in both receivers & transmitters to determine operating frequency.
 - Crystal-controlled oscillator.
 - Variable-frequency oscillator (VFO).

161



Radio Circuits

Oscillators and Amplifiers.

- Amplifiers increase the strength of a signal.
 - Increase voltage, current, or power.
 - Amount of increase is called “gain”.
 - Numeric value – For example, a gain of 10 means the output signal is 10 times bigger than input signal.
 - dB – For example, a power gain of 3 dB means the output signal has twice the power than the input signal.

162

T7A05 -- What is the name of a circuit that generates a signal at a specific frequency?

- A. Reactance modulator
- B. Product detector
- C. Low-pass filter
- D. Oscillator

163



Radio Circuits

Modulators.

- The process of combining information (voice, data, etc.) signals with an RF signal (carrier) is called “modulation”.
 - Can be as simple as an on-off switch.
 - Telegraph key.
 - Can be very complex.
- The circuit that does the modulation is called a “modulator”.

164

T7A08 -- Which of the following describes combining speech with an RF carrier signal?

- A. Impedance matching
- B. Oscillation
- C. Modulation
- D. Low-pass filtering

165



Radio Circuits

Mixers.

- Mixers combine 2 different frequency signals together to produce 4 output frequencies.
 - $f_1 \times f_2 \rightarrow f_1, f_2, f_1-f_2, \text{ \& } f_1+f_2.$
 - Usually only one output frequency wanted, so filters remove the other 3 frequencies.
 - Used in both transmitters & receivers.
- Used to shift a signal or group of signals to another frequency.

166

T7A03 -- Which of the following is used to convert a radio signal from one frequency to another?

- A. Phase splitter
- B. Mixer
- C. Inverter
- D. Amplifier

167



Questions?



168



Technician Class

Next Week

Chapter 4

Propagation, Antennas and Feed Lines