



General License Class

1



General License Class

Chapter 4 Components & Circuits (Part 2)

2



Active Components

Passive Components

- Passive components.
 - Resistors, capacitors, & inductors.
 - Require no external power to function.
 - Simply react to the applied signal.
- Active components.
 - Semiconductors & vacuum tubes.
 - Usually require an external power source.
 - Can modify the applied signal.

3



Active Components

Semiconductor Components

- Semiconductors are materials that do not conduct as well as metals, but better than insulators.
 - Can modify properties by adding controlled amounts of other materials called “dopants”.
- Atomic Structure
 - Nucleus (Protons & Neutrons)
 - Electrons
 - Orbits (Shells)
 - 8 electrons completes a shell


4



Active Components

Semiconductor Components

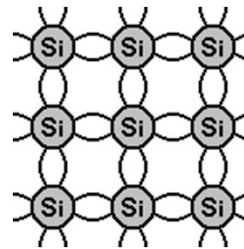- Semiconductor material.
 - 4 electrons in outer shell.
 - Silicon.
 - Germanium.




5



Active Components

Semiconductor Components

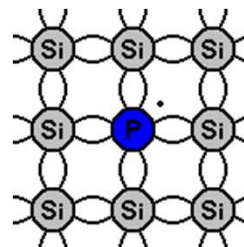- N-type Material.
 - Add an element with 5 electrons in the outer shell (donor Impurity).
 - Arsenic.
 - Antimony.
 - Phosphorus.




6



Active Components

Semiconductor Components

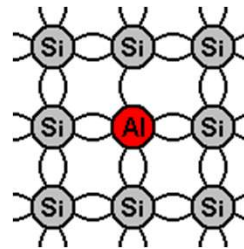- P-type material.
 - Add an element with 3 electrons in the outer shell (acceptor Impurity).
 - Aluminum.
 - Gallium.
 - Indium.



7



Active Components

Semiconductor Components

- Majority Charge Carrier.
 - N-type material = electron.
 - P-type material = hole.

8



Active Components

Semiconductor Components

- Other semiconductor materials.
 - Gallium-Arsenide (GaAs).
 - LED's.
 - Microwave frequencies.
 - Gallium-Arsenide-Phosphide (GaAsP).
 - LED's.


9



Active Components

Semiconductor Components

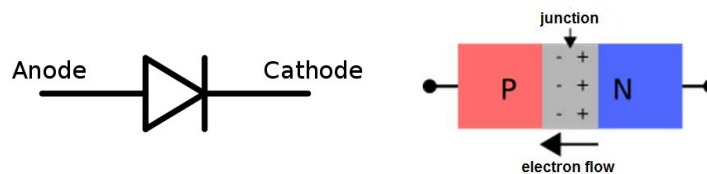- Diodes & Rectifiers.
 - Junction diodes.
 - A P-N junction blocks current flow in one direction & allows current to flow in the other direction.



10



Active Components

Semiconductor Components

- Diodes & Rectifiers.
 - Junction diodes.
 - Voltage applied in the forward direction is called “forward bias”.
 - Large current flow.
 - Voltage applied in the reverse direction is called “reverse bias”.
 - Minimal current flow.

11



Active Components

Semiconductor Components

- Diodes & Rectifiers
 - Diodes designed for low-power signals are called “signal” or “switching” diodes.
 - Diodes designed for high power circuits are often called “rectifiers”.
 - Maximum reverse voltage as high as 1000 V.
 - Maximum forward current as high as 200 A or more.

12



Active Components

Semiconductor Components

- Diodes & Rectifiers.
 - Diode Ratings
 - Peak Inverse Voltage (PIV).
 - Maximum voltage in reverse direction (reverse bias).
 - Maximum Average Forward Current.
 - Maximum Allowable Junction Temperature.

13



Active Components

Semiconductor Components

- Diodes & Rectifiers.
 - Diode Ratings
 - Forward Voltage Drop.
 - Silicon = 0.7 Volts (approx.)
 - Germanium = 0.3 Volts (approx.)
 - GaAs & GaAsP = 1.2 Volts to 1.5 Volts (approx.)

14



Active Components

Semiconductor Components

- Diodes & Rectifiers
 - Diode Types
 - PIN diode.
 - Low forward voltage drop.
 - Used for RF switching & control.

15



Active Components

Semiconductor Components

- Diodes & Rectifiers.
 - Diode Types.
 - Schottky Diode.
 - Low junction capacitance allows operation at VHF & UHF.
 - Lower forward voltage drop.
 - Used as power supply rectifiers.

16



Active Components

Semiconductor Components

- Diodes & Rectifiers.
 - Diode Types.
 - Varactor Diodes (VariCap).
 - Operates with reverse bias.
 - Varying voltage varies junction capacitance.
 - Used for variable-frequency oscillators & for FM modulators.

17



Active Components

Semiconductor Components

- Diodes & Rectifiers
 - Diode Types
 - Zener diode.
 - Operates with reverse bias at the avalanche (breakdown) voltage.
 - Designed to withstand the avalanche current with a proper heat sink.
 - Used as voltage regulators.
 - A large change in the avalanche current results in only a small change in the voltage.

18



Active Components

Semiconductor Components

- Bipolar & Field-Effect Transistors.
 - Adding another layer to a diode creates a device capable of amplifying a signal.
 - The first Transistor was created at Bell Labs in late 1947.



19



Active Components

Semiconductor Components

- Bipolar Transistors.
 - Changing the amount of current (small) flowing through the base-emitter junction controls the amount of current (large) flowing from the collector to the emitter.
 - Bipolar transistors exhibit current gain.
 - $\beta = I_C / I_B$
 - $\alpha = I_C / I_E$


20



Active Components

Semiconductor Components

- Bipolar Transistors.

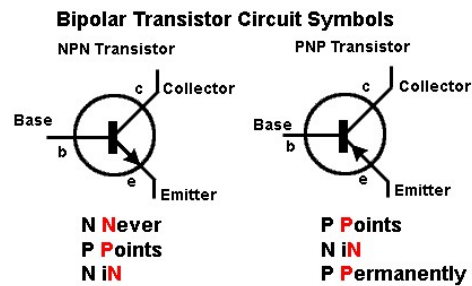


21



Active Components

Semiconductor Components

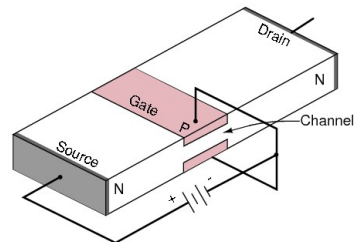- Field-Effect Transistors (FET).
 - Gate voltage controls channel current.
 - Gain measured in Transconductance
 - Siemens
 - High input impedance.
 - Enhancement Mode
 - Depletion Mode




22




Active Components

Semiconductor Components

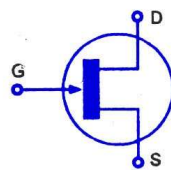- Field-Effect Transistors.
 - Junction Field-Effect Transistor (JFET)



N-Channel JFET

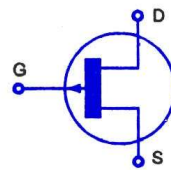

P-Channel JFET

23




Active Components


Semiconductor Components

- Field-Effect Transistors.
 - Metal Oxide Semiconductor Field-Effect Transistor (MOSFET).

NMOS Transistor
(n-channel MOSFET)

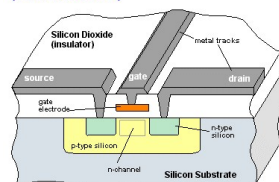

PMOS Transistor
(p-channel MOSFET)

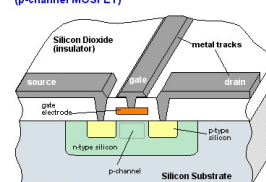


24



Active Components

Semiconductor Components

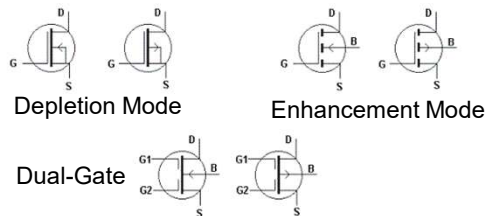- Field-Effect Transistors.
 - Metal Oxide Semiconductor Field-Effect Transistor (MOSFET).



25



Active Components

Semiconductor Components

- Bipolar & Field-Effect Transistors
 - Both bipolar transistors & FET's can be used as switches.
 - Low base current or low gate voltage* puts transistor into "cutoff" -- little or no current flow.
 - Additional reduction of base current or gate voltage does not result in any further reduction in current flow.

**Assuming enhancement-mode FET.*

26



Active Components

Semiconductor Components

- Bipolar & Field-Effect Transistors.
 - High base current or high gate voltage* puts transistor into “saturation” – maximum current flow.
 - Additional increase of base current or gate voltage does not result in any further increase in current flow.

**Assuming enhancement-mode FET.*

27



Active Components


Semiconductor Components

- Bipolar & Field-Effect Transistors.
 - Transistors come in wide variety of packages.
 - Some high-power cases have collector or source directly connected to case.
 - Better heat transfer.
 - **Must be insulated from heat sink or chassis.**

28



Active Components

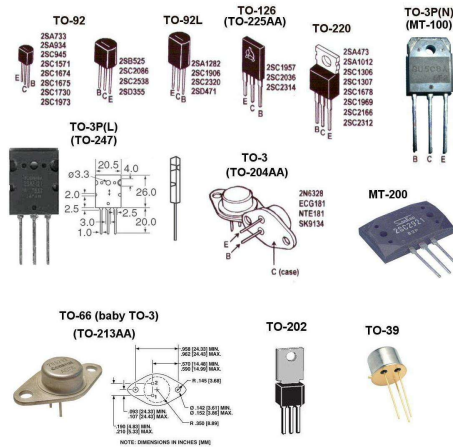


29

G6A03 -- What is the approximate forward threshold voltage of a germanium diode?

- A. 0.1 volt
- ☒ B. 0.3 volts
- C. 0.7 volts
- D. 1.0 volts


30

G6A05 -- What is the approximate forward threshold voltage of a silicon junction diode?

- A. 0.1 volt
- B. 0.3 volts
-  C. 0.7 volts
- D. 1.0 volts

31

G6A07 -- What are the operating points for a bipolar transistor used as a switch?

-  A. Saturation and cutoff
- B. The active region (between cutoff and saturation)
- C. Peak and valley current points
- D. Enhancement and depletion modes

32

G6A09 -- Which of the following describes MOSFET construction?

- A. The gate is formed by a back-biased junction
- B. The gate is separated from the channel by a thin insulating layer
- C. The source is separated from the drain by a thin insulating layer
- D. The source is formed by depositing metal on silicon

33



Active Components

Vacuum Tubes

- Oldest amplification device.
- Invented by Lee De Forest in 1906.




34



Active Components

Vacuum Tubes

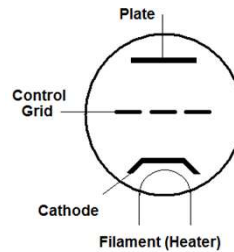- Triode.
 - Simplest tube capable of amplification.
 - 3 Elements
 - Cathode.
 - Control Grid (Grid).
 - Plate (Anode).




35



Active Components

Vacuum Tubes

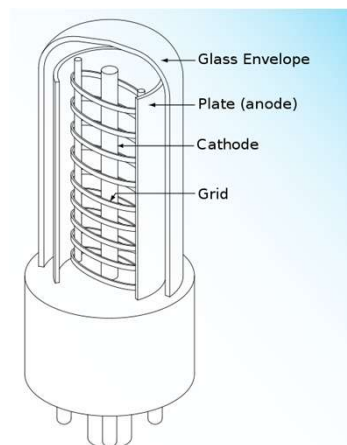- Cathode.
 - Source of electrons.
 - Directly heated.
 - Indirectly heated.
 - At or near ground potential.
 - High current.




36



Active Components

Vacuum Tubes

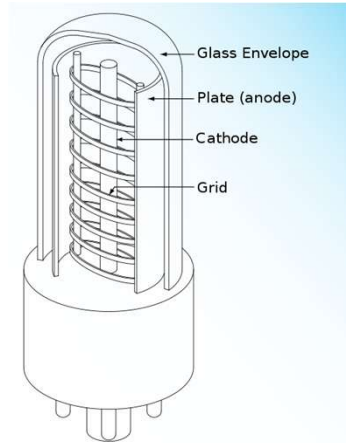- Control Grid (Grid).
 - Fine wire mesh.
 - Controls flow of electrons from cathode to plate.
 - Small negative voltage.
 - Tens of volts.
 - Low current.




37



Active Components

Vacuum Tubes

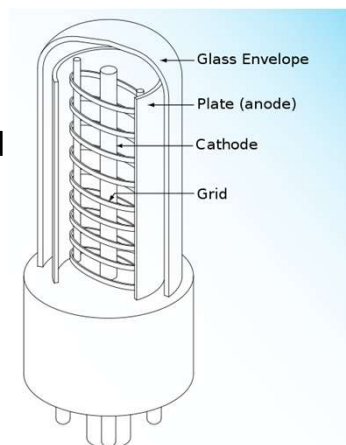- Plate (Anode).
 - Collects electrons emitted by cathode.
 - High positive voltage.
 - Hundreds or thousands of volts.
 - High current.




38



Active Components

Vacuum Tubes

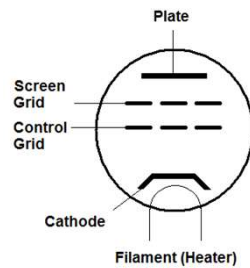- Tetrode.
 - 4 Elements
 - Cathode.
 - Control Grid.
 - Screen Grid.
 - Plate .




39



Active Components

Vacuum Tubes

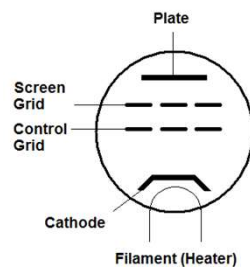- Tetrode.
 - Screen Grid.
 - Reduces capacitance between plate & control grid, preventing self-oscillation.
 - Medium positive voltage.
 - 150-200 Volts.
 - Low Current.




40



Active Components

Vacuum Tubes

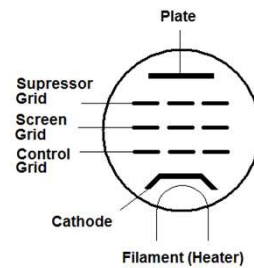- Pentode.
 - 5 Elements
 - Cathode.
 - Control Grid.
 - Screen Grid.
 - Suppressor Grid.
 - Plate.




41



Active Components

Vacuum Tubes

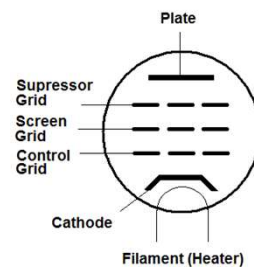- Pentode.
 - Suppressor Grid.
 - Reduces “splashback” of electrons from plate to screen grid.
 - At or near cathode potential.
 - Often directly connected to cathode.
 - Low current.



42



Active Components

Vacuum Tubes



43

G6A10 -- Which element of a vacuum tube regulates the flow of electrons between cathode and plate?

- A. Control grid
- B. Suppressor grid
- C. Screen grid
- D. Trigger electrode

44

G6A12 -- What is the primary purpose of a screen grid in a vacuum tube?

- A. To reduce grid-to-plate capacitance
B. To increase efficiency
C. To increase the control grid resistance
D. To decrease plate resistance

45



Active Components

Analog & Digital Integrated Circuits

- Many transistors, diodes, & interconnections can be made on a single silicon wafer almost as easily as a single transistor.
 - The result is called an "integrated circuit" or "IC".



46



Active Components

Analog & Digital Integrated Circuits

- Analog integrated circuits.
 - Used for amplification, filtering, voltage regulation, and many other applications.
 - Operational Amplifier.
 - Linear Voltage Regulator.


47



Active Components

Analog & Digital Integrated Circuits

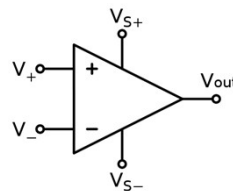- Analog integrated circuits.
 - Operational Amplifier.
 - Circuit characteristics totally controlled by external components.
 - Amplifiers.
 - Active filters.
 - Adding signals.




48



Active Components

Analog & Digital Integrated Circuits

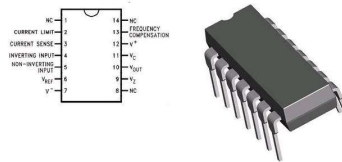- Analog integrated circuits.
 - Linear Voltage Regulators.
 - LM-723.
 - External Components required.



49



Active Components

Analog & Digital Integrated Circuits

- Analog integrated circuits.
 - Linear Voltage Regulators.
 - IC 3-Terminal Regulators.
 - Thermal shutdown.
 - Overvoltage protection.
 - Foldback current limiting.
 - LM78Lxx -- 100 mA.
 - LM78xx -- 1 Amp.
 - LM78Hxx -- 3 Amps.



50



Active Components

Analog & Digital Integrated Circuits

- Digital integrated circuits.
 - Binary (base2) number system used for digital processing.
 - Only digits 0 & 1 are used.
 - Any number can be represented by a string of 0's & 1's.
 - 0 = 000, 1 = 001, 2 = 010, 3 = 011, 4 = 100, etc.
 - "0" & "1" can be easily represented by the "off" & "on" states of a transistor or similar device.


51



Active Components

Analog & Digital Integrated Circuits

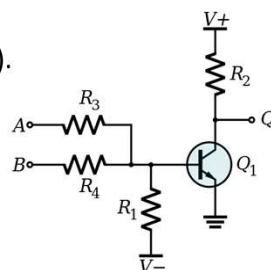- Digital integrated circuits.
 - Logic Families.
 - Resistor-Transistor-Logic (RTL).
 - 1st digital logic family (1961).
 - High power consumption.
 - No longer used.
 - Replaced by DTL.




52



Active Components

Analog & Digital Integrated Circuits

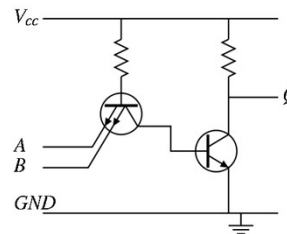- Digital integrated circuits.
 - Logic Families.
 - Transistor-Transistor-Logic (TTL).
 - Replaced RTL & DTL.
 - +5V supply voltage.
 - Low noise immunity.




53



Active Components

Analog & Digital Integrated Circuits

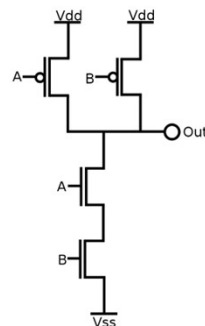- Digital integrated circuits.
 - Logic Families.
 - Complimentary Metal-Oxide Semiconductor (CMOS).
 - Replacing TTL.
 - +5V - 15V supply voltage.
 - High noise immunity.




54



Active Components

Analog & Digital Integrated Circuits

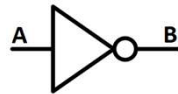- Digital Logic Basics.
 - Basic building block of a digital circuit is called a “gate”.
 - NOT (inverting) gate.
 - AND gate.
 - OR gate.



55



Active Components

Analog & Digital Integrated Circuits

- Digital Logic Basics.
 - One-input elements.
 - Non-inverting buffer.
 - Inverting buffer or “Not” gate.


56




Active Components

Analog & Digital Integrated Circuits

- Buffer & Inverting Buffer (NOT gate).

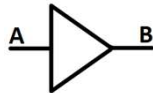

A	B
0	0
1	1

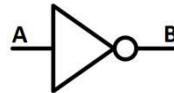

A	B
0	1
1	0

57



Active Components

Analog & Digital Integrated Circuits

- Digital Logic Basics.
 - AND gate.
 - Output true only if **ALL** inputs are true
 - NAND (Not-AND) gate.
 - Output false only if **ALL** inputs are true.

58



Active Components

Analog & Digital Integrated Circuits

- AND gate and NAND gate.



A	B	C
0	0	0
0	1	0
1	0	0
1	1	1



A	B	C
0	0	1
1	0	1
0	1	1
1	1	0

59



Active Components

Analog & Digital Integrated Circuits

- Digital Logic Basics.
 - OR gate.
 - Output true if one or more of the inputs are true.
 - NOR (Not-OR) gate.
 - Output false if one or more of the inputs are true.

60



Active Components

Analog & Digital Integrated Circuits

- OR gate and NOR gate.



A	B	C
0	0	0
0	1	1
1	0	1
1	1	1



A	B	C
0	0	1
1	0	0
0	1	0
1	1	0

61



Active Components

Analog & Digital Integrated Circuits

- Digital Logic Basics.
 - XOR (Exclusive-OR) gate.
 - Output true if one and only one of the inputs is true.
 - XNOR (Exclusive-NOR) gate.
 - Output false if one and only one of the inputs is true.

62



Active Components

Analog & Digital Integrated Circuits

- XOR gate and XNOR gate.



A	B	C
0	0	0
0	1	1
1	0	1
1	1	0



A	B	C
0	0	1
1	0	0
0	1	0
1	1	1

63



Active Components

Analog & Digital Integrated Circuits

- Digital Logic Basics.
 - Sequential logic
 - Current state dependent on both current inputs and previous state.
 - Must include some form of "memory".

64



Active Components

Analog & Digital Integrated Circuits

- Digital Logic Basics.
 - Flip-flop
 - a.k.a -- Bi-stable multivibrator, latch.
 - Several different types.
 - S-R, J-K, D, T.
 - Gated, non-gated.
 - Clocked, non-clocked.
 - Can be used as frequency divider.
 - Can be used as frequency counter.

65




Active Components

Analog & Digital Integrated Circuits

- Digital Logic Basics.
 - Set-Reset (SR) Latch
 - Most basic latch type.

S	R	Action
0	0	No change
0	1	Q = 0
1	0	Q = 1
1	1	Forbidden

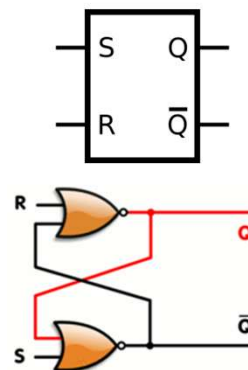

66



Active Components

Analog & Digital Integrated Circuits

- Digital Logic Basics.
 - J-K flip-flop
 - Adds toggle function to SR latch.
 - Must be clocked.

67




Active Components

Analog & Digital Integrated Circuits

- Digital Logic Basics.
 - J-K flip-flop.

Clock (>)	J	K	Action
0	--	--	No change
1	0	0	No change
1	0	1	Q = 0
1	1	0	Q = 1
1	1	1	Toggle (Q = not Q)

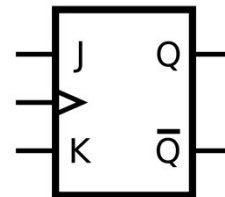


68



Active Components

Analog & Digital Integrated Circuits

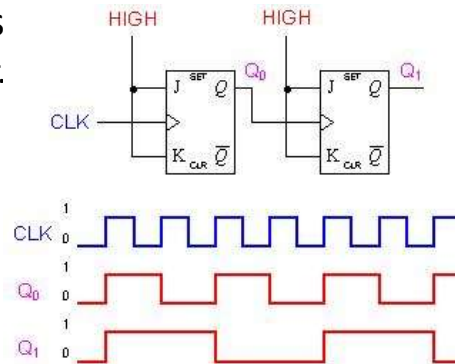- Digital Logic Basics
 - Frequency divider.



69




Active Components

Analog & Digital Integrated Circuits

- Digital Logic Basics.
 - D flip-flop
 - Most common type.
 - Computer RAM.
 - Must be clocked.

Clock (>)	D	Action
0	--	No change
1	0	Q = 0
1	1	Q = 1

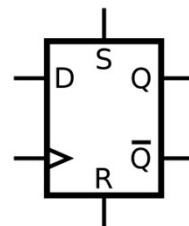


70



Active Components

Analog & Digital Integrated Circuits

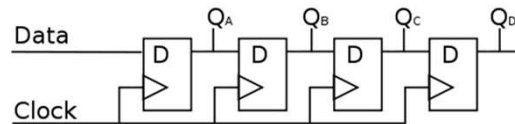- Digital Logic Basics.
 - Shift Register
 - Cascaded D flip-flops.
 - Shifts data from stage to stage.
 - Converts serial data to parallel data.
 - Converts parallel data to serial data.



71




Active Components

Analog & Digital Integrated Circuits

- Digital Logic Basics.
 - T flip-flop
 - Toggles state with each clock pulse.
 - D flip-flop with Q output connected to D input.

Clock (>)	T	Action
0	--	No change
1	0	No change
1	1	Toggle (Q = not Q)

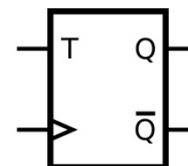


72



Active Components

Analog & Digital Integrated Circuits

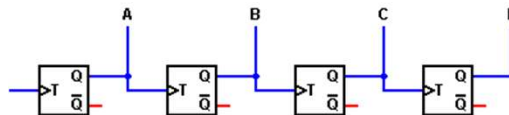- Digital Logic Basics.
 - Digital Counter
 - Cascaded T flip-flops.
 - Counts number of input pulses.
 - Number of states = 2^N where N = number of stages.
 - For example: 3-stage counter has 8 states.




73



Active Components


RF Integrated Circuits

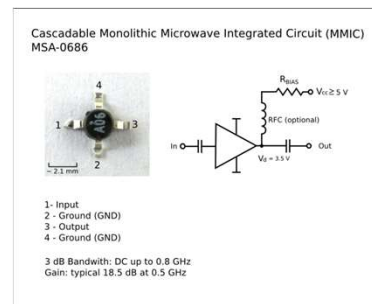- Monolithic Microwave Integrated Circuit (MMIC).
 - VHF, UHF, microwaves.
 - Typically 50Ω.
 - Low Noise Figure.
 - 3.5 dB to 6.0 dB.
 - Microstrip construction.




74

G6B02 -- What is meant by the term MMIC?

- A. Multi-Mode Integrated Circuit
-  B. Monolithic Microwave Integrated Circuit
- C. Metal Monolayer Integrated Circuit
- D. Mode Modulated Integrated Circuit


75

G6B03 -- Which of the following is an advantage of CMOS integrated circuits compared to TTL integrated circuits?

-  A. Low power consumption
- B. High power handling capability
- C. Better suited for RF amplification
- D. Better suited for power supply regulation


76

G6B06 -- What kind of device is an integrated circuit operational amplifier?

- A. Digital
- B. MMIC
- C. Programmable Logic
-  D. Analog


77

G7B03 -- Which of the following describes the function of a two-input AND gate?

- A. Output is high when either or both inputs are low
-  B. Output is high only when both inputs are high
- C. Output is low when either or both inputs are high
- D. Output is low only when both inputs are high


78

G7B05 -- How many states does a 3-bit binary counter have?

- A. 3
- B. 6
-  C. 8
- D. 16

79

G7B06 -- What is a shift register?

-  A. A clocked array of circuits that passes data in steps along the array
- B. An array of operational amplifiers used for tri-state arithmetic operations
- C. A digital mixer
- D. An analog mixer

80



Active Components

Microprocessors & Related Components

- Microprocessor.
 - A computer on a chip.
 - Thousands of gates.
 - Tens of thousands of transistors & diodes.




81



Active Components

Microprocessors & Related Components

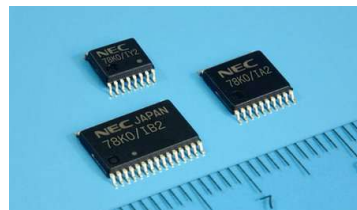- Microcontroller.
 - Microprocessor with added interfaces to input & output devices.




82



Active Components

Microprocessors & Related Components

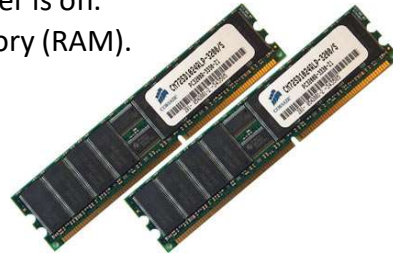- Memory.
 - Volatile.
 - Data is lost when power is off.
 - Random Access Memory (RAM).



83



Active Components

Microprocessors & Related Components

- Memory.
 - Non-Volatile.
 - Data is retained when power is off.
 - Read-Only Memory (ROM).
 - Programmable Read-Only Memory (PROM).



84



Active Components

Microprocessors & Related Components

- Memory.
 - Non-Volatile.
 - Erasable Programmable Read-Only Memory (EPROM).
 - Electrically Erasable Programmable Read-Only Memory (EEPROM).



85



Active Components

Microprocessors & Related Components

- Interfaces.
 - Serial interfaces.
 - One bit transferred at a time.
 - RS-232 (COM ports).
 - Commonly used to connect amateur transceivers to personal computers.
 - Becoming obsolete.

86



Active Components

Microprocessors & Related Components

- Interfaces.
 - Serial interfaces.
 - Universal Serial Bus (USB).
 - Replacing RS-232.
 - Commonly used to connect amateur transceivers to personal computers.
 - Ethernet.

87



Active Components

Microprocessors & Related Components

- Data Interfaces.
 - Common serial interfaces.

Interface Type	Maximum Data Transfer Speed
RS-232	115 kilobits/second
USB 1.0	1.5 megabits/second
USB 2.0	480 megabits/second
USB 3.0	5 gigabits/second
Firewire	800 megabits/second

88



Active Components

Microprocessors & Related Components

- Interfaces.
 - Parallel interfaces.
 - Multiple bits transferred at a time.
 - Used for connections to mass storage devices.
 - Integrated Drive Electronics (IDE)
 - Small Computer System Interface (SCSI)
 - Centronics® Parallel Printer Port.
 - Being replaced by high-speed serial interfaces.

89



Active Components

Microprocessors & Related Components

- Visual Interfaces.
 - Indicator.
 - Displays on/off state of a single item.
 - Incandescent Lamp.
 - Largely replaced by LED's.



90



Active Components

Microprocessors & Related Components

- Visual Interfaces.
 - Indicator.
 - Light-Emitting-Diode (LED).
 - Emits light when forward biased.
 - Faster than incandescent lamp.
 - Less power than incandescent lamp.
 - Less heat than incandescent lamp.
 - Longer life than incandescent lamp.

91



Active Components

Microprocessors & Related Components

- Visual Interfaces.
 - Indicator.
 - Light-Emitting-Diode (LED).



92



Active Components

Visual Interfaces

- Display.
 - Displays text or graphical information.
 - Most common type in amateur equipment is the liquid crystal display (LCD).
 - Requires illumination.
 - Ambient light.
 - Back light.


93



Active Components

Visual Interfaces.

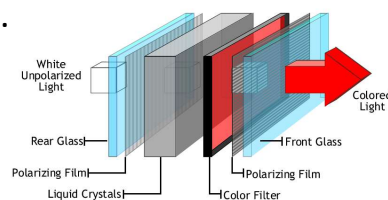- Liquid-Crystal Displays
 - Rotates the polarization of the light passing through it.
 - Applying a voltage across the crystal changes the polarization.



94

G6B08 -- How is an LED biased when emitting light?

- A. In the tunnel-effect region
- B. At the Zener voltage
- C. Reverse biased
- D. Forward biased

95



Break




96



Practical Circuits

Rectifiers & Power Supplies

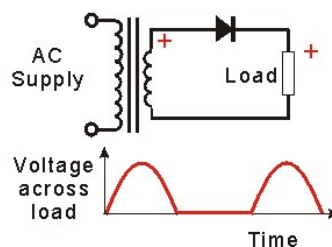- Rectifier Circuits.
 - Half-Wave Rectifier.
 - Only one-half of the cycle (180°) delivers power to the load.




97



Practical Circuits

Rectifiers & Power Supplies

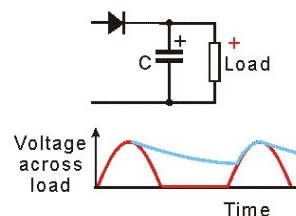- Rectifier Circuits.
 - Half-Wave Rectifier.
 - Creates a series of widely-spaced pulses at the frequency of the input voltage.
 - Very difficult to filter.
 - $V_{Avg} = 0.45 \times V_{AC}$
 - Diode PIV $\geq 2 \times V_p$
 - Diode $I_{Max} \geq I_{Load}$




98



Practical Circuits

Rectifiers & Power Supplies

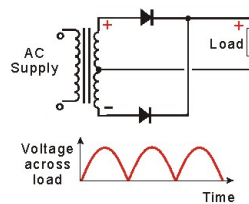- Rectifier Circuits.
 - Full-Wave Rectifier.
 - The entire cycle (360°) delivers power to the load.




99



Practical Circuits

Rectifiers & Power Supplies

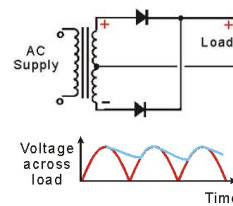- Rectifier Circuits.
 - Full-Wave Rectifier.
 - Creates a series of closely-spaced pulses at twice the frequency of the input voltage.
 - Easier to filter.
 - $V_{Avg} = 0.9 \times V_{AC}$
 - Diode PIV $\geq 2 \times V_p$
 - Diode $I_{Max} \geq 0.5 \times I_{Load}$




100



Practical Circuits

Rectifiers & Power Supplies

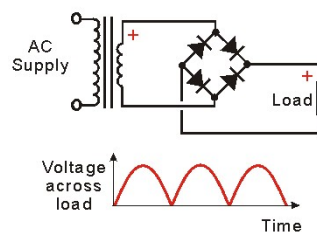- Rectifier Circuits.
 - Full-Wave Bridge Rectifier.
 - The entire cycle (360°) delivers power to the load.




101



Practical Circuits

Rectifiers & Power Supplies

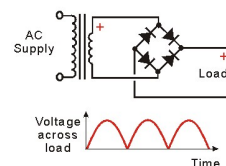- Rectifier Circuits.
 - Full-Wave Bridge Rectifier.
 - Creates a series of closely-spaced pulses at twice the frequency of the input voltage.
 - Easier to filter.
 - $V_{Avg} = 0.9 \times V_{AC}$
 - Diode $PIV \geq V_p$
 - Diode $I_{Max} \geq 0.5 \times I_{Load}$



102



Practical Circuits

Rectifiers & Power Supplies

- Rectifier Circuits.

Type of Circuit	Diode PIV Rating	Diode Current Rating
Half-Wave Rectifier	$\geq 2 \times V_p$	$\geq I_{Load}$
Full-Wave Center-Tapped	$\geq 2 \times V_p$	$\geq 0.5 \times I_{Load}$
Full-Wave Bridge	$\geq V_p$	$\geq 0.5 \times I_{Load}$

103



Practical Circuits

Rectifiers & Power Supplies

- Rectifier Circuits.
 - Diodes in parallel.
 - Diodes can be connected in parallel to increase current capacity, **ONLY** if you put a small-value resistor in series with each diode to equalize the currents between each diode.

104



Practical Circuits

Rectifiers & Power Supplies

- Rectifier Circuits.
 - Diodes in series.
 - Diodes can be connected in series to increase voltage capacity, **ONLY** if you put a large-value resistor in parallel with each diode to equalize the voltage across each diode.

105



Practical Circuits

Rectifiers & Power Supplies

- Power Supply Filter Circuits.
 - The output from a rectifier is a series of pulses unsuitable for operating electronic equipment.
 - Need a filter after the rectifier to smooth pulses into a steady DC voltage.
 - A low-pass filter with a cut-off frequency well below the frequency of the pulses.
 - Half-wave rectifier → 60 Hz pulses.
 - Full-wave rectifier → 120 Hz pulses.


106



Practical Circuits

Rectifiers & Power Supplies

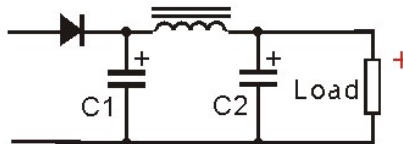- Power Supply Filter Circuits.
 - An R-C or L-C network after the rectifier to reduce the variations in the DC output voltage.
 - Variations are called “ripple”.
 - $\text{Ripple} = 100 \times V_{AC(P-P)} / V_{DC}$



107



Practical Circuits

Rectifiers & Power Supplies

- Power Supply Filter Circuits.
 - Choosing the capacitors.
 - Large capacitance.
 - Low effective series resistance (ESR).
 - Computer-grade aluminum electrolytic.
 - Large capacitances & low ESR in smaller case sizes.



108



Practical Circuits

Rectifiers & Power Supplies

- Power Supply Filter Circuits.
 - Choosing the inductor.
 - Large inductance.
 - Low series resistance.
 - Not always used.
 - A capacitor alone may provide sufficient filtering, especially if the load is a voltage regulator.



109



Practical Circuits

Rectifiers & Power Supplies

- Power Supply Safety.
 - **EVERY** power supply should have:
 - A fuse in the AC input line.
 - An on/off switch in the AC input line.
 - A bleeder resistor.
 - A high value resistor connected across the output of the power supply.
 - Discharges the filter capacitors when power is removed.

110



Practical Circuits

Rectifiers & Power Supplies

- Switchmode or Switching Power Supplies.
 - The AC input voltage is rectified & fed to a solid-state oscillator.
 - The oscillator generates series of high-frequency pulses.
 - 20 kHz or greater.

111



Practical Circuits

Rectifiers & Power Supplies

- Switchmode or Switching Power Supplies.
 - The pulses are applied to the primary winding of a transformer.
 - The output from the secondary winding is rectified, filtered, & sent to the load.
 - The output voltage regulated by varying the width of the pulses fed to the transformer.


112



Practical Circuits

Rectifiers & Power Supplies

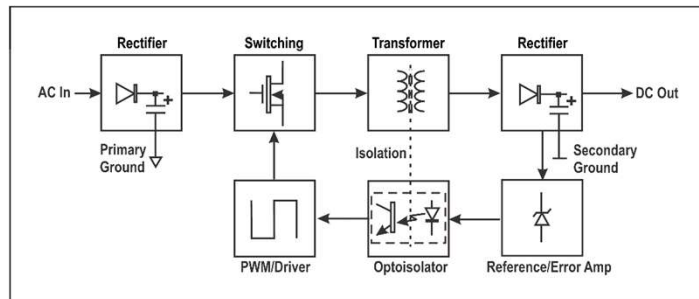- Switchmode or Switching Power Supplies.



113



Practical Circuits

Rectifiers & Power Supplies

- Switchmode or Switching Power Supplies.
 - The high switching frequency allows:
 - The use of a much smaller transformer.
 - The use of much smaller capacitors.
 - The use of much smaller inductors.
 - A rapid response to load changes.

114



Practical Circuits

Rectifiers & Power Supplies

- Switchmode or Switching Power Supplies.
 - Advantages over linear power supplies.
 - Smaller size.
 - Less weight.
 - Higher efficiency.
 - Disadvantages over linear power supplies.
 - RF noise generation.
 - Higher cost.


115

G7A01 -- What is the function of a power supply bleeder resistor?

- A. It acts as a fuse for excess voltage
- B. It discharges the filter capacitors when power is removed
- C. It removes shock hazards from the induction coils
- D. It eliminates ground loop current


116

G7A02 -- Which of the following components are used in a power supply filter network?

- A. Diodes
- B. Transformers and transducers
-  C. Capacitors and inductors
- D. All these choices are correct


117

G7A03 -- Which type of rectifier circuit uses two diodes and a center-tapped transformer?

-  A. Full-wave
- B. Full-wave bridge
- C. Half-wave
- D. Synchronous


118

G7A04 -- What is characteristic of a half-wave rectifier in a power supply?

-  A. Only one diode is required
- B. The ripple frequency is twice that of a full-wave rectifier
- C. More current can be drawn from the half-wave rectifier
- D. The output voltage is two times the peak output voltage of the transformer


119

G7A05 -- What portion of the AC cycle is converted to DC by a half-wave rectifier?

- A. 90 degrees
-  B. 180 degrees
- C. 270 degrees
- D. 360 degrees


120

G7A06 -- What portion of the AC cycle is converted to DC by a full-wave rectifier?

- A. 90 degrees
- B. 180 degrees
- C. 270 degrees
-  D. 360 degrees

121

G7A07 -- What is the output waveform of an unfiltered full-wave rectifier connected to a resistive load?

-  A. A series of DC pulses at twice the frequency of the AC input
- B. A series of DC pulses at the same frequency as the AC input
- C. A sine wave at half the frequency of the AC input
- D. A steady DC voltage

122

G7A08 -- Which of the following is characteristic of a switchmode power supply as compared to a linear power supply?

- A. Faster switching time makes higher output voltage possible
- B. Fewer circuit components are required
- C. High-frequency operation allows the use of smaller components
- D. Inherently more stable



123



Practical Circuits

Batteries & Chargers

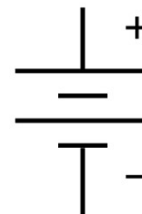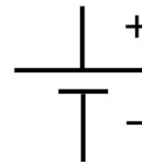- Batteries.
 - Batteries produce energy by an electrochemical reaction.
 - Batteries are used by amateurs for:
 - Hand-Held operations.
 - Portable operations.
 - Mobile operations.
 - Emergency operations.



124



Practical Circuits

Batteries & Chargers

- Batteries.
 - There are two different categories of batteries:
 - Primary.
 - Electrochemical reaction is **not** reversible.
 - Battery **cannot** be recharged.
 - Secondary.
 - Electrochemical reaction **is** reversible.
 - Battery **can** be recharged.

125



Practical Circuits

Batteries & Chargers

- Batteries.
 - Primary.
 - Examples:
 - Carbon-Zinc
 - Alkaline.
 - Silver-Nickel.
 - Lithium.
 - Silver-Oxide.



126



Practical Circuits

Batteries & Chargers

- Batteries.
 - Secondary.
 - Examples:
 - Lead-Acid.
 - Nickel-Cadmium (NiCad).
 - Nickel-Metal-Hydrate (NiMH).
 - Lithium-Ion (Li-Ion).



127



Practical Circuits

Batteries & Chargers

- Batteries.
 - Should be discharged at a low rate.
 - Less internal heating.
 - NiCad & NiMH batteries have low internal resistance & are designed for high discharge currents.

128



Practical Circuits

Batteries & Chargers

- Batteries.
 - All batteries have some leakage.
 - Self-discharge.
 - Store in cool, dry location.
 - 12-volt lead-acid batteries should not be discharged below 10.5 volts.

129



Practical Circuits

Batteries & Chargers

- Charging Batteries.
 - **NEVER** attempt to recharge a primary-cell battery.
 - **ALWAYS** use correct charger.
 - NiCad & NiMH batteries are charged with constant current until voltage rises to specified value.
 - Lead-Acid batteries are charged with constant voltage until current drops to specified value.

130



Practical Circuits

Batteries & Chargers

- Charging Batteries.
 - **ALWAYS** provide proper ventilation.
 - Lead-Acid batteries produce hydrogen gas during charging.
(Remember the Hindenburg!)



131



Practical Circuits

Alternative Power

- Solar Power.
 - Photovoltaic conversion.
 - If sufficient light falls on a P-N junction, free electrons in the N-type material will absorb energy & flow across the junction into the P-type material producing an electric current.




132



Practical Circuits

Alternative Power

- Solar Power

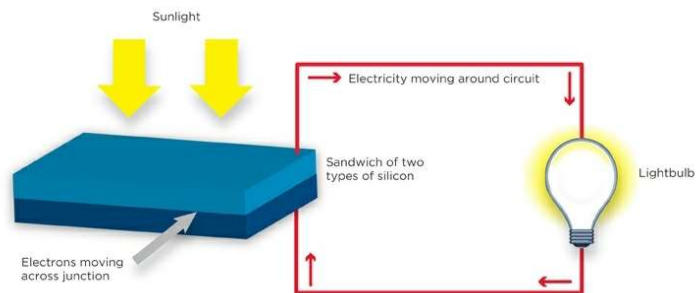

133



Practical Circuits

Alternative Power

- Solar Power.
 - Solar cells.
 - The most common material is Silicon.
 - The most efficient material is Gallium-Arsenide.
 - A fully-illuminated junction yields about 0.5 VDC.
 - Solar cell can produce almost 1 kW/m².
 - Solar power is rapidly becoming commercially viable for power generation.

134



Practical Circuits

Alternative Power

- Solar Power.
 - Solar panels.
 - To create a solar panel, individual cells are connected in series to produce the desired output voltage and then connected in parallel to provide the desired output current.


135



Practical Circuits

Alternative Power

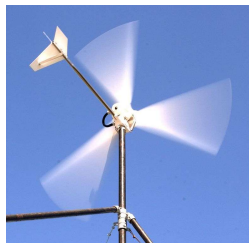- Wind Power
 - A DC generator attached to a propeller.



136



Practical Circuits

Alternative Power

- Energy Storage.
 - Solar power & wind power are not continuously available.
 - Must store energy during periods of daylight or when the wind is blowing to save up for nighttime or when the wind is calm.

137



Practical Circuits

Alternative Power

- Energy Storage.
 - Storage batteries are most commonly used.
 - A solar system must have a diode in series between the solar panel & the batteries to prevent discharging batteries back through the panel during low-light conditions.

138



Practical Circuits

Alternative Power

- Energy Storage.
 - A solar system using lithium-ion phosphate batteries for storage must use a charge controller to prevent over-charging the batteries.
 - Over-charging can create a safety hazard.
 - Over-charging can cause battery damage.
 - Over-charging can shorten battery life.


139

G4E08 -- In what configuration are the individual cells in a solar panel connected together?

- A. Series-parallel
- B. Shunt
- C. Bypass
- D. Full-wave bridge


140

G4E09 -- What is the approximate open-circuit voltage from a fully illuminated silicon photovoltaic cell?

- A. 0.02 VDC
-  B. 0.5 VDC
- C. 0.2 VDC
- D. 1.38 VDC


141

G4E10 -- Why should a series diode be connected between a solar panel and a storage battery that is being charged by the panel?

- A. To prevent overload by regulating the charging voltage
-  B. To prevent discharge of the battery through the panel during times of low or no illumination
- C. To limit the current flowing from the panel to a safe value
- D. To prevent damage to the battery due to excessive voltage at high illumination levels


142

G4E11 -- What precaution should be taken when connecting a solar panel to a lithium iron phosphate battery?

- A. Ground the solar panel outer metal framework
- B. Ensure the battery is placed terminals-up
- C. A series resistor must be in place
-  D. The solar panel must have a charge controller

143

G6A01 -- What is the minimum allowable discharge voltage for maximum life of a standard 12 volt lead-acid battery?

- A. 6 volts
- B. 8.5 volts
-  C. 10.5 volts
- D. 12 volts

144

G6A02 -- What is an advantage of batteries with low internal resistance?

- A. Long life
- ➔ B. High discharge current
- C. High voltage
- D. Rapid recharge

145



Practical Circuits

Connectors

- Convenient way to make electrical connections.
- Terminology.
 - Pins = Contacts that extend out of connector body.
 - Sockets = Hollow, recessed contacts.
 - Connectors with pins are “male”.
 - Connectors with sockets are “female”.

146



Practical Circuits

Connectors

- Terminology (cont'd).
 - Connectors with specially-shaped bodies or pin/socket arrangements are call “keyed connectors”.
 - Keyed connectors avoid damage caused by mismatching connectors.
 - Plugs = Connectors installed on ends of cables.
 - Jacks = Connectors installed on equipment.


147



Practical Circuits

Connectors

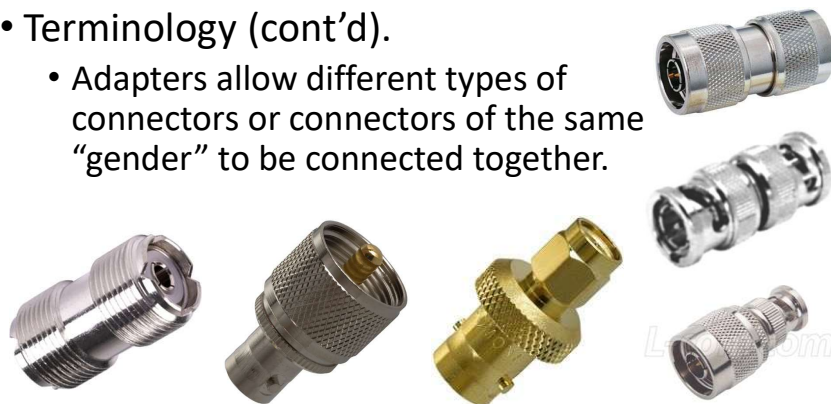- Terminology (cont'd).
 - Adapters allow different types of connectors or connectors of the same “gender” to be connected together.




148



Practical Circuits

• Connectors

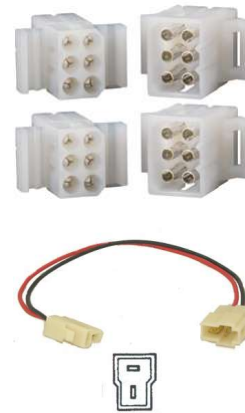- Power Connectors.
 - Molex® Connectors.
 - Many HF transceivers use the 6-pin connector.
 - Pins may be paralleled to increase current capacity.
 - Many VHF/UHF transceivers use the 2-pin connector.



149



Practical Circuits

Connectors

- Power Connectors.
 - Coaxial Power Connectors.
 - Low current.
 - Commonly used on hand-held transceivers and station accessories.
 - Available with different diameter center pins.



150



Practical Circuits

Connectors

- Power Connectors.
 - Anderson PowerPole® Connectors.
 - Becoming increasingly popular for station power connections.
 - Easy to install with proper crimp tool.



151



Practical Circuits

Connectors

- Power Connectors.
 - Terminal Strips.



152



Practical Circuits

Connectors

- Audio and Control Connectors.
 - Phone plugs & jacks (TRS connectors).
 - Audio.
 - Keys.
 - Control signals.



153



Practical Circuits

Connectors

- Audio and Control Connectors.
 - Phone plugs & jacks (TRS connectors).
 - Sizes:
 - Standard -- 1/4" (6.35 mm) dia.
 - Aircraft -- 0.206" dia. (Rare).
 - Miniature -- 1/8" (3.5 mm) dia.
 - Sub-miniature -- 3/32" (2.5 mm) dia.

154



Practical Circuits

Connectors

- Audio and Control Connectors.
 - RCA Phono plugs & jacks.
 - Audio.
 - Low-level RF.
 - Control Signals.




155



Practical Circuits

Connectors

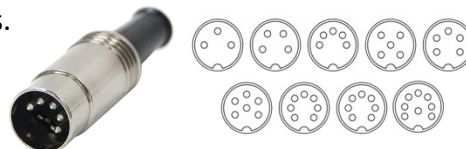- Audio and Control Connectors.
 - DIN connectors.
 - *Deutsches Institut für Normung*
 - German national standards organization.
 - Audio.
 - Control Signals.




156



Practical Circuits

Connectors

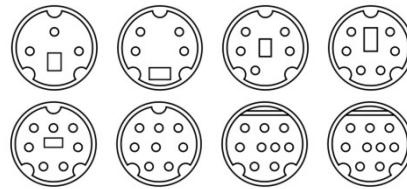- Audio and Control Connectors.
 - Mini-DIN connectors.
 - Audio.
 - Control Signals.



157



Practical Circuits

Connectors

- 8-pin round connector.
 - a.k.a. -- Foster connector.
 - Commonly used as a microphone connector.



158



Practical Circuits

Connectors

- RF Connectors.
 - UHF.
 - Plug = PL-259.
 - Socket = SO-239.
 - ≤ 150 MHz.
 - ≥ 1.5 kW.
 - ≤ 500 V_{Peak}.



159



Practical Circuits

Connectors

- RF Connectors.
 - UHF.
 - Non-constant impedance.
 - Not weather resistant.
 - Relatively inexpensive.



160



Practical Circuits

Connectors

- RF Connectors.
 - N.
 - ≤ 10 GHz.
 - ≥ 1.5 kW.
 - ≤ 1500 V_{Peak}
 - Constant impedance.
 - 50 Ω or 75 Ω versions available.
 - Weather-resistant.
 - More expensive than UHF connectors.



161



Practical Circuits

Connectors

- RF Connectors.
 - BNC.
 - ≤ 4 GHz.
 - Low power.
 - ≤ 500 V_{Peak}
 - Constant impedance.
 - 50 Ω or 75 Ω versions available.



162



Practical Circuits

Connectors

- RF Connectors.
 - SMA.
 - ≤ 18 GHz.
 - Low Power
 - ≤ 250 V_{RMS}
 - Constant impedance.
 - 50Ω .



163



Practical Circuits

Connectors

- Data Connectors.
 - D-Subminiature Connectors.
 - DB-25
 - Serial (COM) ports.
 - Parallel printer ports.
 - DE-9
 - Incorrectly called a DB-9.
 - Serial (COM) ports.



164



Practical Circuits

Connectors

- Data Connectors.
 - USB Connectors.
 - USB replacing RS-232.
 - Many manufacturers are making devices to interconnect transceivers & other station equipment using USB.



165

G6B04 -- What is a typical upper frequency limit for low SWR operation of 50-ohm BNC connectors?

- A. 50 MHz
- B. 500 MHz
- ☒ C. 4 GHz
- D. 40 GHz

166

G6B07 -- Which of the following describes a type N connector?

- A. A moisture-resistant RF connector useful to 10 GHz
- B. A small bayonet connector used for data circuits
- C. A low noise figure VHF connector
- D. A nickel plated version of the PL-259

167

G6B11 -- What is an SMA connector?

- A. A type-S to type-M adaptor
- B. A small threaded connector suitable for signals up to several GHz
- C. A connector designed for serial multiple access signals
- D. A type of push-on connector intended for high-voltage applications

168

G6B12 -- Which of these connector types is commonly used for low frequency or dc signal connections to a transceiver?

- A. PL-259
- B. BNC
- C. RCA Phono
- D. Type N

169



Basic Test Equipment

Analog & Digital Meters

- Multimeters.
 - a.k.a. – VOM, DVM, DMM, VTVM.
 - Measures:
 - Voltage.
 - Current.
 - Resistance.



170



Basic Test Equipment

Analog & Digital Meters

- Multimeters.
 - Accuracy expressed in % of full scale.
 - If accuracy is 2% of full scale on 100 mA scale, then accuracy is ± 2 mA.
 - Resolution expressed in digits.
 - Typically $3\frac{1}{2}$ digits (0.000 to 1.999)
 - $3\frac{1}{2}$ digit \rightarrow 0.05% resolution.
- **DO NOT CONFUSE RESOLUTION WITH ACCURACY!**



171



Basic Test Equipment

Analog & Digital Meters

- For accurate results, meters should have little or no effect on the circuit being measured.
 - A voltmeter should have the highest input impedance as possible.
 - An ammeter should have the lowest series resistance as possible.



172



Basic Test Equipment

Analog & Digital Meters

- Multimeters.
 - Analog.
 - D'Arsonval movement.
 - Rotating coil suspended between magnets.
 - When current flows in coil, coil rotates moving needle across scale.
 - Coil impedance affects accuracy.
 - Sensitivity expressed in Ohms/Volt.
 - 20,000 Ω/V = very good analog voltmeter.

173



Basic Test Equipment

Analog & Digital Meters

- Multimeters.
 - Analog.



174



Basic Test Equipment

Analog & Digital Meters

- Multimeters.
 - Vacuum Tube Voltmeters.
 - D'Arsonval movement.
 - Used a vacuum tube amplifier to improve sensitivity.
 - Typically 10 meg Ω /V or greater.



175



Basic Test Equipment

Analog & Digital Meters

- Multimeters
 - Digital Meters.
 - Uses a high input impedance FET amplifier to improve sensitivity.
 - Typically 10 M Ω /V or greater.
 - Uses internal microprocessor to perform measurement calculations.



176



Basic Test Equipment

Analog & Digital Meters

- Analog Meters.
 - Faster response times
 - Easier to use when adjusting a circuit.
 - e.g., Tuning an amplifier.
- Digital Meters.
 - Higher sensitivity.
 - Higher resolution.



177



Basic Test Equipment

Oscilloscope

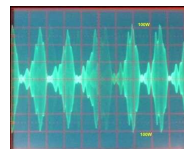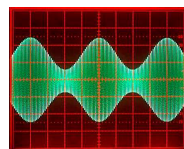- Real-time display of rapidly-changing audio or RF signals.
 - Keying waveform of CW signal.
- Voltage measurements of complex waveforms.



178



Basic Test Equipment

Oscilloscope

- Displays voltage versus time.
 - The signal to be displayed is applied to the vertical deflection plates.
 - A sawtooth waveform from a time base is applied to the horizontal deflection plates.

179



Basic Test Equipment

Oscilloscope

- The bandwidth of the vertical amplifier determines the highest frequency signal that can be displayed.
- Sometimes there are 2 or more vertical amplifiers.
 - Allows displaying multiple signals simultaneously.

180



Basic Test Equipment

Impedance & Resonance Measurements

- Antenna analyzer.
 - Measures:
 - Impedance.
 - Resistance.
 - Reactance.
 - Standing-wave-ratio (SWR).



181



Basic Test Equipment

Impedance & Resonance Measurements

- Antenna analyzer.
 - Can also measure:
 - Cable velocity factor.
 - Cable electrical length.
 - Distance to fault.
 - Susceptible to interference from strong nearby transmitters.



182



Basic Test Equipment

Field Strength & RF Power Meters

- Field Strength Meters.
 - Measures relative strength of RF field.
 - Determine antenna pattern.
 - Close-in direction finding.





183



Basic Test Equipment

Field Strength & RF Power Meters

- Field Strength Meters.

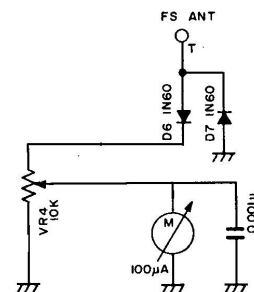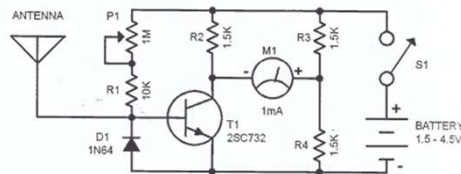

184



Basic Test Equipment

Field Strength & RF Power Meters

- RF Power Meters.
 - Directional Wattmeter.
 - Measure forward power.
 - Measure reflected power.
 - Calculate SWR.



185

G4B01 -- What item of test equipment contains horizontal and vertical channel amplifiers?

- A. An ohmmeter
- B. A signal generator
- C. An ammeter
- D. An oscilloscope

186

G4B02 -- Which of the following is an advantage of an oscilloscope versus a digital voltmeter?

- A. An oscilloscope uses less power
- B. Complex impedances can be easily measured
- C. Greater precision
- D. Complex waveforms can be measured


187

G4B03 -- Which of the following is the best instrument to use for checking the keying waveform of a CW transmitter?

- A. An oscilloscope
- B. A field strength meter
- C. A sidetone monitor
- D. A wavemeter


188

G4B04 -- What signal source is connected to the vertical input of an oscilloscope when checking the RF envelope pattern of a transmitted signal?

- A. The local oscillator of the transmitter
- B. An external RF oscillator
- C. The transmitter balanced mixer output
-  D. The attenuated RF output of the transmitter


189

G4B05 -- Why do voltmeters have high input impedance?

- A. It improves the frequency response
- B. It allows for higher voltages to be safely measured
- C. It improves the resolution of the readings
-  D. It decreases the loading on circuits being measured


190

G4B06 -- What is an advantage of a digital voltmeter as compared to an analog voltmeter?

- A. Better for measuring computer circuits
- B. Less prone to overload
-  C. Higher precision
- D. Faster response


191

G4B09 -- When is an analog multimeter preferred to a digital multimeter?

- A. When testing logic circuits
- B. When high precision is desired
- C. When measuring the frequency of an oscillator
-  D. When adjusting circuits for maximum or minimum values


192

G4B10 -- Which of the following can be determined with a directional wattmeter?

-  A. Standing wave ratio
- B. Antenna front-to-back ratio
- C. RF interference
- D. Radio wave propagation

193

G4B11 -- Which of the following must be connected to an antenna analyzer when it is being used for SWR measurements?

- A. Receiver
- B. Transmitter
-  C. Antenna and feed line
- D. All these choices are correct

194

G4B12 -- What effect can strong signals from nearby transmitters have on an antenna analyzer?

- A. Desensitization which can cause intermodulation products which interfere with impedance readings
- B. Received power that interferes with SWR readings
- C. Generation of harmonics which interfere with frequency readings
- D. All these choices are correct

195

G4B13 -- Which of the following can be measured with an antenna analyzer?

- A. Front-to-back ratio of an antenna
- B. Power output from a transmitter
- C. Impedance of coaxial cable
- D. Gain of a directional antenna

196



Questions?



197



General License Class

Next Week

Chapter 5

**Radio Signals &
Equipment**

198